

# Computer Organization: Boolean Logic



# Representing and Manipulating Data

## Last Unit

---

- How to represent data as a sequence of bits
- How to interpret bit representations
- Use of levels of abstraction in representing more complex information (music, pictures) using simpler building blocks (numbers)

## This Unit

---

- How sequences of bits are implemented using electrical signals, and manipulated by circuits
- Use of levels of abstraction in designing more complex computer components from simpler components

# Foundations

Boolean logic is the logic of digital circuits

# Implementing Bits

- Computers compute by manipulating electricity according to specific rules.
- We associate electrical signals inside the machine with bits. Any electrical device with two distinct states (e.g. on/off switch, two distinct voltage or current levels) could implement our bits.
- The rules are implemented by electrical circuits.

# Conceptualizing bits and circuits

- **ON** or **1**: **true**
- **OFF** or **0**: **false**
- circuit behavior: expressed in *Boolean logic* or *Boolean algebra*

# Boolean Logic (Algebra)

- Computer circuitry works based on Boolean Logic (Boolean Algebra) : operations on True (1) and False (0) values.

A	B	$A \wedge B$ (A AND B) (conjunction)	$A \vee B$ (A OR B) (disjunction)
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

A	$\neg A$ (NOT A) (negation)
0	1
1	0

- A and B in the table are Boolean variables, AND and OR are operations (also called functions).

# Foundations of Digital Computing

- Boolean Algebra was invented by George Boole in 1854 (before digital computers)
  - Variables and functions take on only one of two possible values: True (1) or False (0).
- The correspondence between Boolean Logic and circuits was not discovered until 1930s
  - Shannon's thesis: A Symbolic Analysis of Relay and Switching Circuits argued that electrical applications of Boolean Algebra could construct any logical, numerical relationship.
  - We forget about the *logical* (truth and falsehood) aspect of Boolean logic and just manipulate symbols.

# Boolean Logic & Truth Tables

- Example: You can think of  $A \wedge B$  below as *15110 is fun and 15110 is useful* where A stands for the statement *15110 is fun*, B stands for the statement *15110 is useful*.

A	B	$A \wedge B$ (A AND B) (conjunction)	$A \vee B$ (A OR B) (disjunction)
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

A	$\neg A$ (NOT A) (negation)
0	1
1	0






# Logic gates

the basic elements of digital circuits

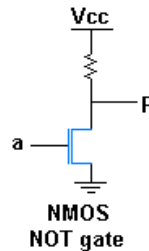
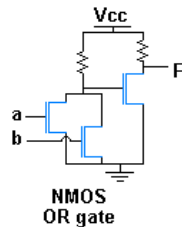
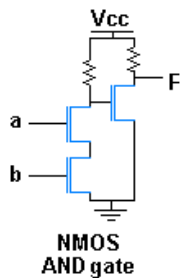
# Logic Gates

- A gate is a physical device that implements a Boolean operator by performing basic operations on electrical signals.
- Nowadays, gates are built from transistors.



physical picture of gates

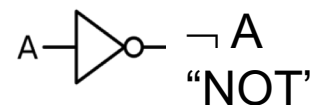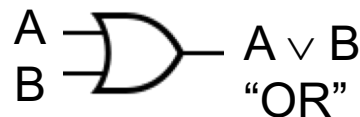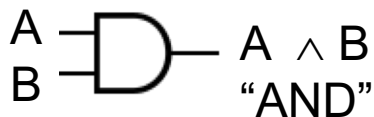Physical behavior of circuits is beyond the scope of our course.







logical picture of gates

# A Mechanical Implementation
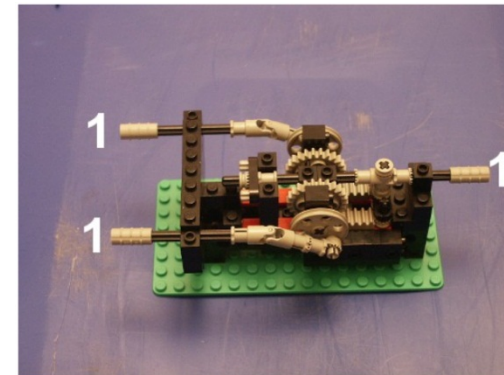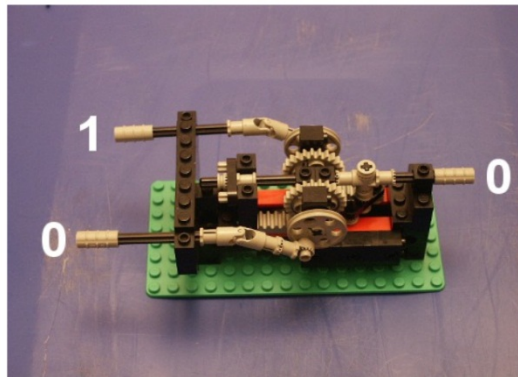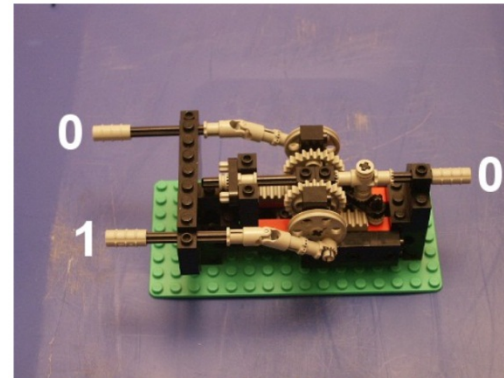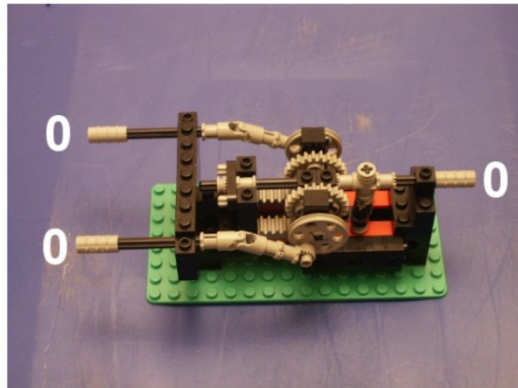
## Push-pull logic AND gate

- For an input pushed-in lever represents 1
- For an output pushed-in lever represents 0




Source:  
[randomwraith.com](http://randomwraith.com)  
by Martin Howard

# Combinational circuits

combinations of logic gates

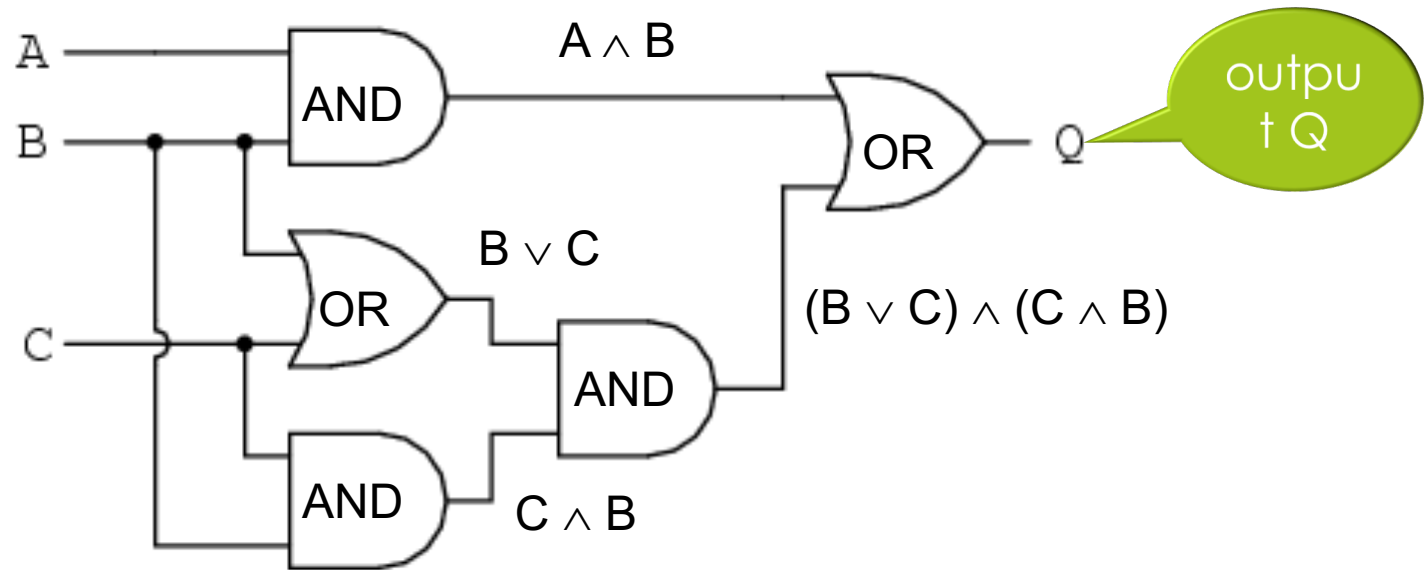
# Combinational Circuits

The logic states of inputs at any given time determine the state of the outputs.



What is Q?  $(A \wedge B) \vee ((B \wedge C) \wedge (C \wedge B))$

# Truth Table of a Circuit

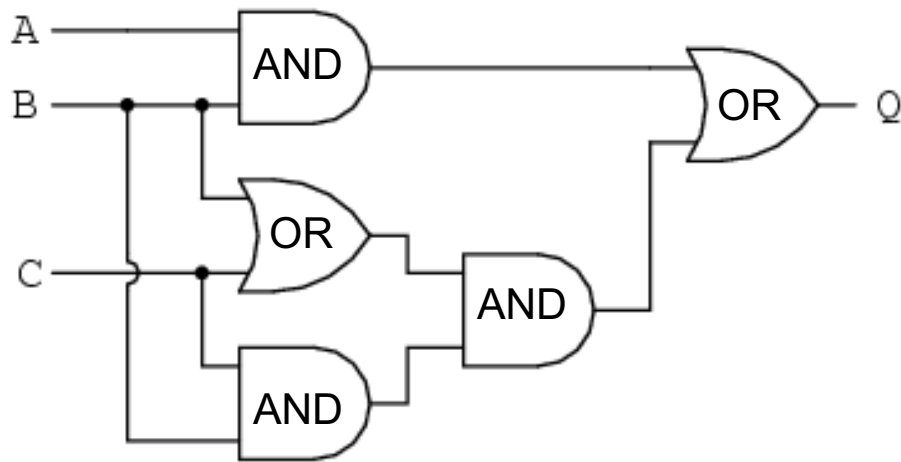


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

How do I know that there should be 8 rows in the truth table?

Describes the relationship between inputs and outputs of a device

# Truth Table of a Circuit

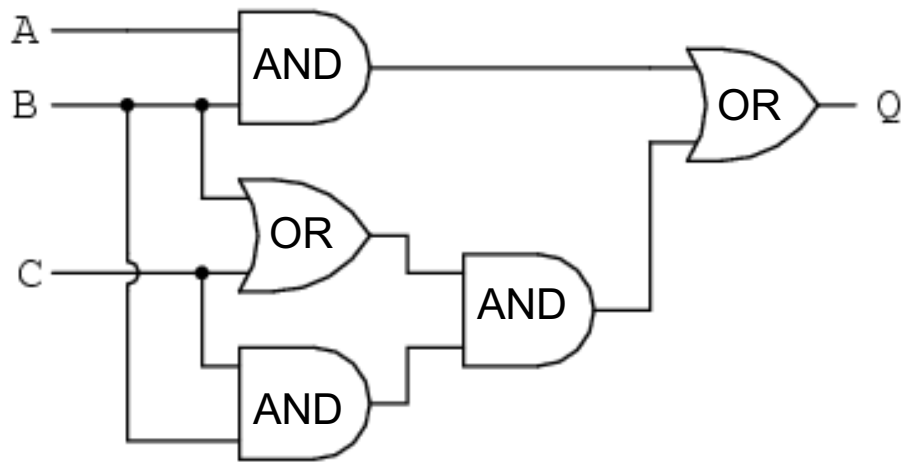


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Describes the relationship between inputs and outputs of a device

# Truth Table of a Circuit

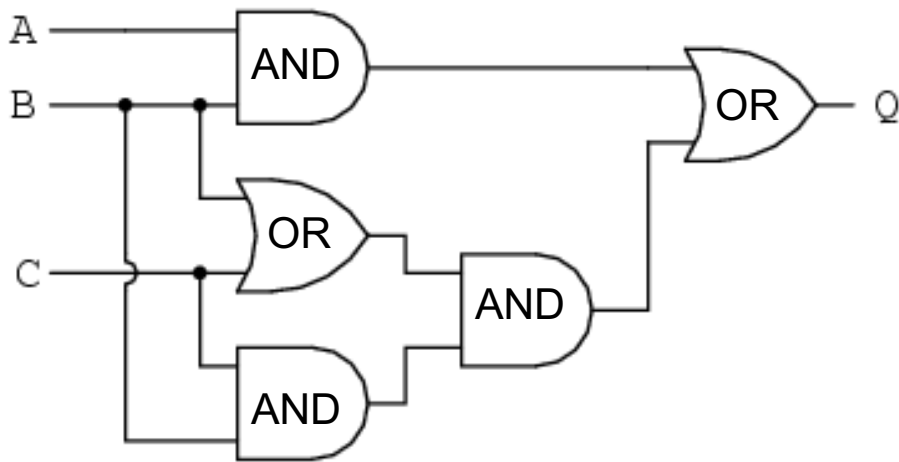


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Describes the relationship between inputs and outputs of a device



# Truth Table of a Circuit

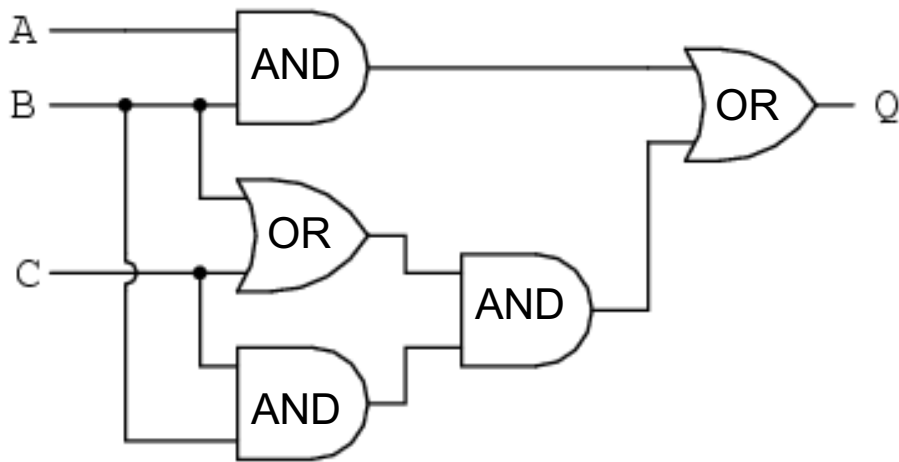


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Describes the relationship between inputs and outputs of a device

# Truth Table of a Circuit

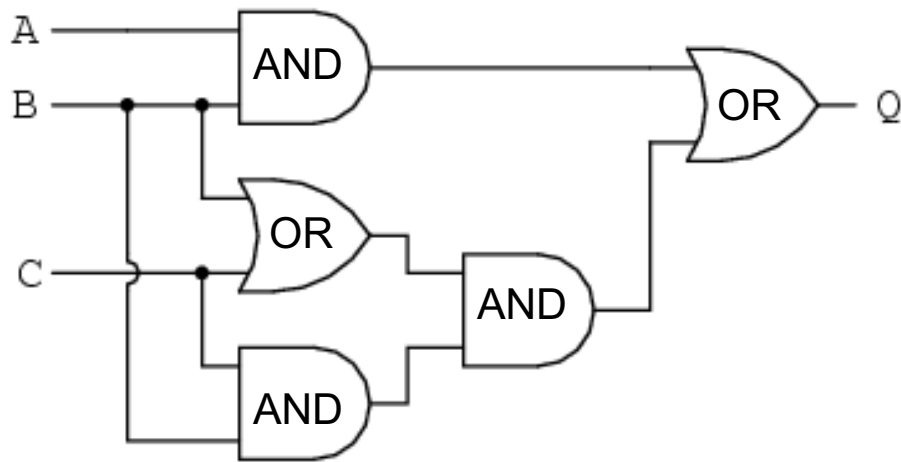


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Describes the relationship between inputs and outputs of a device

# Truth Table of a Circuit

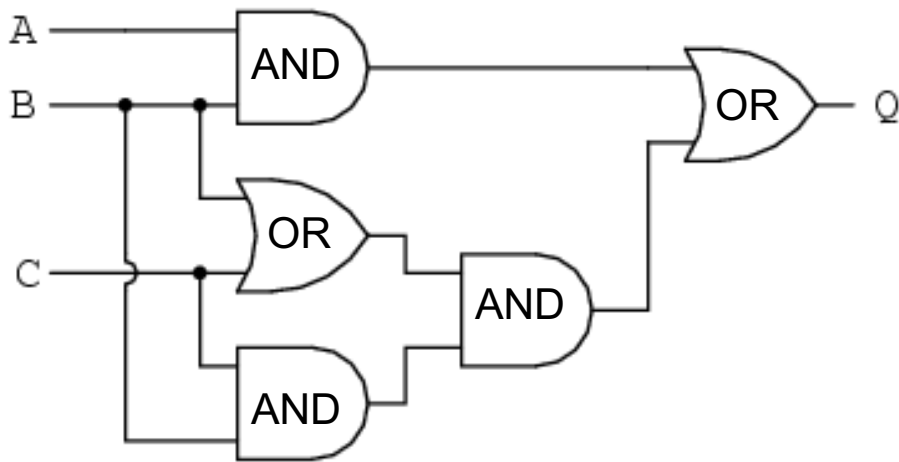


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	
1	1	0	
1	1	1	

Describes the relationship between inputs and outputs of a device

# Truth Table of a Circuit

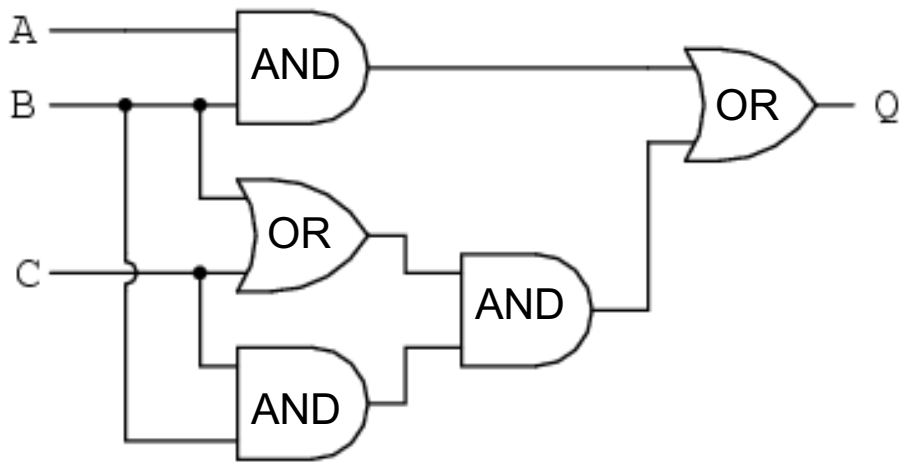


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	
1	1	1	

Describes the relationship between inputs and outputs of a device

# Truth Table of a Circuit

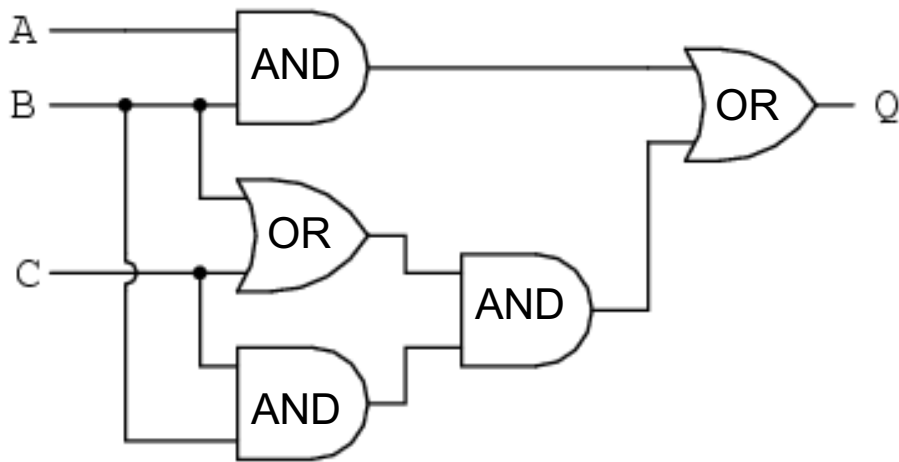


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	

Describes the relationship between inputs and outputs of a device

# Truth Table of a Circuit

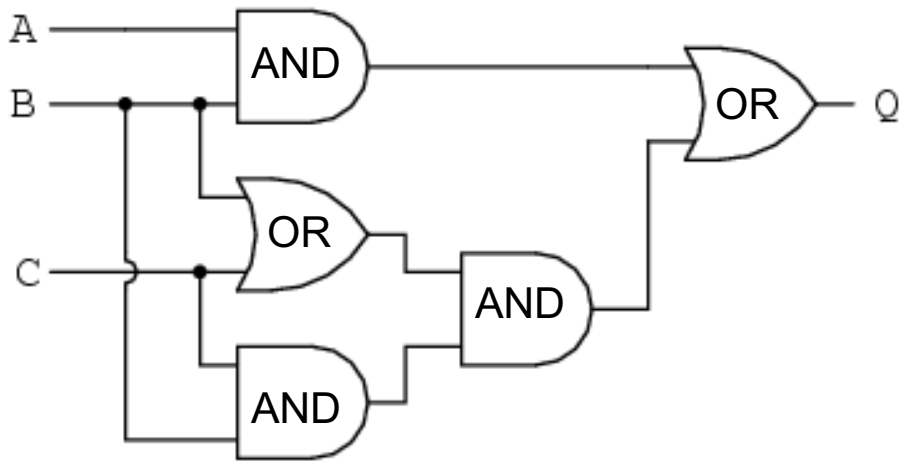

$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Describes the relationship between inputs and outputs of a device

# Describing Behavior of Circuits

- Boolean expressions
- Circuit diagrams
- Truth tables



Equivalent notations

# Manipulating circuits


Boolean algebra and logical equivalence



# Why manipulate circuits?

- The design process
  - simplify a complex design for easier manufacturing, faster or cooler operation, ...
- Boolean algebra helps us find another design guaranteed to have same behavior

# Logical Equivalence

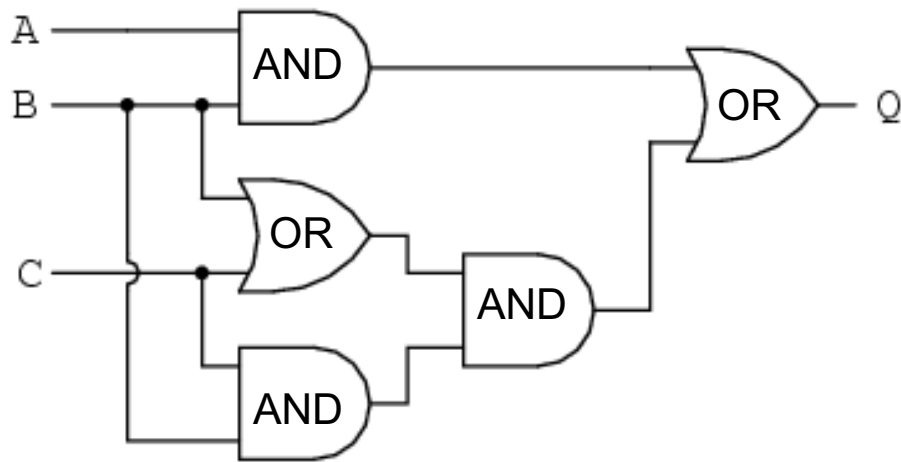


$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Can we come up with a simpler circuit implementing the same truth table? Simpler circuits are typically cheaper to produce, consume less energy etc.

# Logical Equivalence

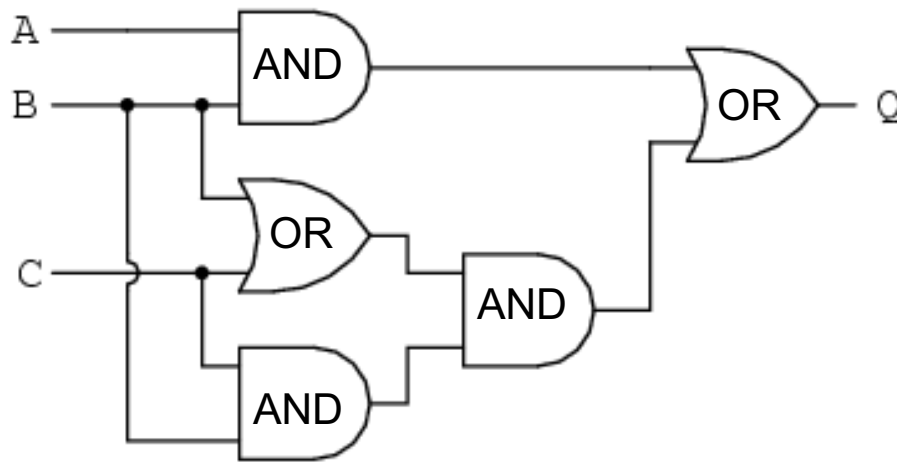

$$Q = (A \wedge B) \vee ((B \vee C) \wedge (C \wedge B))$$

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

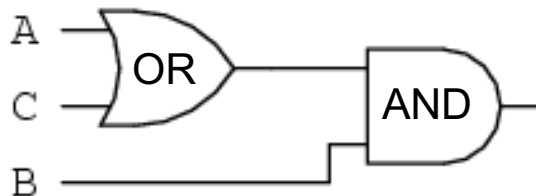

$$Q = B \wedge (A \vee C)$$

This smaller circuit is logically equivalent to the one above: they have the same truth table. By using laws of Boolean Algebra we convert a circuit to another equivalent circuit.

# Laws for the Logical Operators $\wedge$ and $\vee$ (Similar to $\times$ and $+$ )

- Commutative:  $A \wedge B = B \wedge A$                        $A \vee B = B \vee A$
- Associative:  $A \wedge B \wedge C = (A \wedge B) \wedge C = A \wedge (B \wedge C)$   
 $A \vee B \vee C = (A \vee B) \vee C = A \vee (B \vee C)$
- Distributive:  $A \wedge (B \vee C) = (A \wedge B) \vee (A \wedge C)$   
 $A \vee (B \wedge C) = (A \vee B) \wedge (A \vee C)$
- Identity:  $A \wedge 1 = A$                                        $A \vee 0 = A$
- Dominance:  $A \wedge 0 = 0$                                        $A \vee 1 = 1$
- Idempotence:  $A \wedge A = A$                                        $A \vee A = A$
- Complementation:  $A \wedge \neg A = 0$                                        $A \vee \neg A = 1$
- Double Negation:  $\neg \neg A = A$

# Laws for the Logical Operators $\wedge$ and $\vee$ (Similar to $\times$ and $+$ )

□ Commutative:  $A \wedge B = B \wedge A$                        $A \vee B = B \vee A$

□ Associative:  $A \wedge B \wedge C = (A \wedge B) \wedge C = A \wedge (B \wedge C)$   
 $A \vee B \vee C = (A \vee B) \vee C = A \vee (B \vee C)$

□ Distributive:  $A \wedge (B \vee C) = (A \wedge B) \vee (A \wedge C)$   
 $A \vee (B \wedge C) = (A \vee B) \wedge (A \vee C)$

← Not true for  
+ and  $\times$

□ Identity:  $A \wedge 1 = A$                        $A \vee 0 = A$

The A's and B's here are schematic variables! You can instantiate them with any expression that has a Boolean value:

$$(x \vee y) \wedge z = z \wedge (x \vee y) \text{ (by commutativity)}$$

$$\underbrace{A} \wedge \underbrace{B} = \underbrace{B} \wedge \underbrace{A}$$

# Applying Properties for $\wedge$ and $\vee$

Showing  $(x \wedge y) \vee ((y \vee z) \wedge (z \wedge y)) = y \wedge (x \vee z)$

Commutativity  $A \wedge B = B \wedge A$

$$(x \wedge y) \vee ((z \wedge y) \wedge (y \vee z))$$

Distributivity  $A \wedge (B \vee C) = (A \wedge B) \vee (A \wedge C)$

$$(x \wedge y) \vee (z \wedge y \wedge y) \vee (z \wedge y \wedge z)$$

Associativity, Commutativity, Idempotence

$$(x \wedge y) \vee ((z \wedge y) \vee (y \wedge z))$$

Commutativity, idempotence  $A \wedge A = A$

$$(y \wedge x) \vee (y \wedge z)$$

Distributivity (backwards)  $(A \wedge B) \vee (A \wedge C) = A \wedge (B \vee C)$

$$y \wedge (x \vee z)$$

**Conclusion:**

$$(x \wedge y) \vee ((y \vee z) \wedge (z \wedge y)) = y \wedge (x \vee z)$$


# Extending the system

more gates and DeMorgan's laws


# More gates (NAND, NOR, XOR)

A	B	A nand B	A nor B	A xor B
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	0

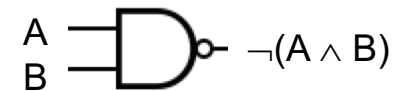
□ nand (“not and”):  $A \text{ nand } B = \text{not } (A \text{ and } B)$



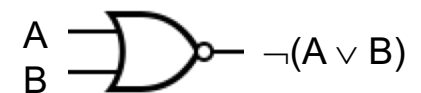□ nor (“not or”):  $A \text{ nor } B = \text{not } (A \text{ or } B)$



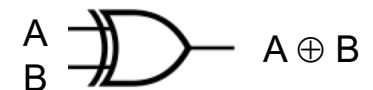□ xor (“exclusive or”):  
 $A \text{ xor } B = (A \text{ and not } B) \text{ or } (B \text{ and not } A)$





# A curious fact

- Functional Completeness of NAND and NOR
  - Any logical circuit can be implemented using NAND gates only
- Same applies to NOR

# DeMorgan's Law

Nand:  $\neg(A \wedge B) = \neg A \vee \neg B$

Nor:  $\neg(A \vee B) = \neg A \wedge \neg B$

# DeMorgan's Law

Nand:  $\neg(A \wedge B) = \neg A \vee \neg B$

`if not (x > 15 and x < 110): ...`

is logically equivalent to

`if (not x > 15) or (not x < 110): ...`

Nor:  $\neg(A \vee B) = \neg A \wedge \neg B$

`if not (x < 15 or x > 110): ...`

is logically equivalent to

`if (not x < 15) and (not x > 110): ...`

# A circuit for parity checking


Boolean expressions and circuits

# A Boolean expression that checks parity

- 3-bit odd parity checker F: an expression that should be true when the count of 1 bits is odd: when 1 or 3 of the bits are 1s.

$$P = (\neg A \wedge \neg B \wedge C) \vee (\neg A \wedge B \wedge \neg C) \vee (A \wedge \neg B \wedge \neg C) \vee (A \wedge B \wedge C)$$

A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

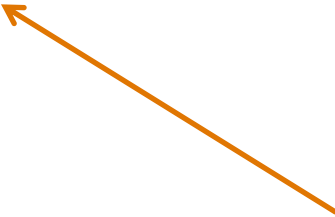

There are specific methods for obtaining canonical Boolean expressions from a truth table, such as writing it as a disjunction of conjunctions or as a conjunction of disjunctions.

Note we have four subexpressions above each of them corresponding to exactly one row of the truth table where P is 1.

# The circuit


## 3-bit odd parity checker

$$P = (\neg A \wedge \neg B \wedge C) \vee (\neg A \wedge B \wedge \neg C) \vee (A \wedge \neg B \wedge \neg C) \vee (A \wedge B \wedge C)$$

A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$P = (A \oplus B) \oplus C$$

logically  
equivalent

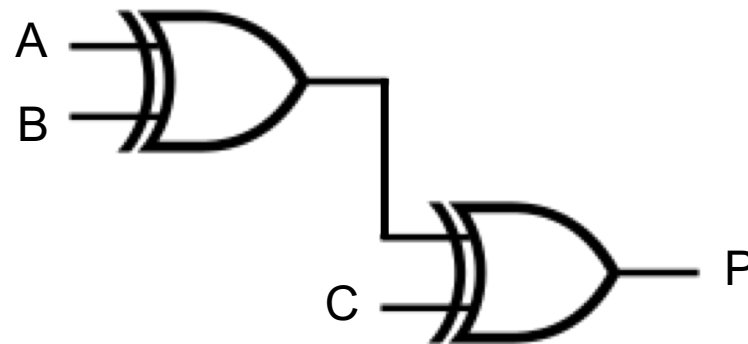

# Summary

You should be able to:

- Identify basic gates
- Describe the behavior of a gate or circuit using Boolean expressions, truth tables, and logic diagrams
- Transform one Boolean expression into another given the laws of Boolean algebra

# Next Time

- How circuits are combined to form a computer
- Von Neumann architecture revisited
- Fetch – Decode - Execute Cycle

