

10.20 The rotor shown in Figure P10.20 is driven by a torque $\tau_o(t)$. The rotor has a moment of inertia J , but the friction is negligible. The field winding is excited by a constant voltage source, resulting in a constant magnetic flux. The armature resistance is denoted by R_A , and the armature inductance is negligible. Use (29) to obtain expressions for e_m and τ_e .

- a) With the rotor initially at rest and with the switch in the left-hand position connecting the armature to a short circuit, the applied torque is $\tau_o(t) = U(t)$. Find and sketch ω as a function of time.
- b) After the rotor has reached a steady-state speed under the conditions of part (a), the switch is thrown to the right, thereby connecting the armature to the battery. Find and sketch ω versus t if a constant unit torque continues to be applied to the rotor.

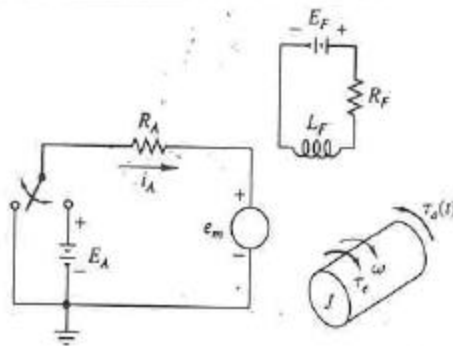


FIGURE P10.20

- c) After a new steady-state speed has been reached under the conditions of part (b), the applied torque is removed, with the switch still in the right-hand position. Again find and sketch ω versus t .

Refer to equation (29)

$$\tau_e = d i_A \quad (1)$$

$$e_m = \alpha \omega \quad (2)$$

a) Switch in left hand position

Equation for armature circuit is:

$$R_A i_A + e_m = 0 \quad \text{or using (2)}$$

$$R_A i_A + \alpha \omega = 0 \quad (3)$$

The equation of motion for the rotor is

$$J\dot{\omega} = +\tau_e - \tau_a \quad (4)$$

or using (1)

$$J\dot{\omega} - \alpha i_A = -\tau_a \quad (5)$$

$$(3) \Rightarrow i_A = -\frac{\alpha \omega}{R_A}$$

$$J\dot{\omega} + \frac{\alpha^2 \omega}{R_A} = -\tau_a \quad (6)$$

Assume $\tau_a = U(t)$, $\omega(0) = 0$

Take Laplace T.

$$J s \Omega(s) + \frac{\alpha^2}{R_A} \Omega(s) = -\frac{1}{s}$$

$$\Omega(s) = -\frac{1}{s} \cdot \frac{1}{s + \frac{\alpha^2}{R_A J}} \quad (7)$$

use Partial Fractions

$$\Omega(s) = \frac{A}{s} + \frac{B}{s + \frac{\alpha^2}{R_A J}}$$


$$A = -\frac{1}{J} \cdot \frac{1}{\frac{\alpha^2}{R_A J}} = -\frac{R_A}{\alpha^2}$$

$$B = +\frac{1}{J \frac{\alpha^2}{R_A J}} = \frac{R_A}{\alpha^2}$$

$$\therefore \Omega(s) = \frac{R_A}{\alpha^2} \left(-\frac{1}{s} + \frac{1}{s + \frac{\alpha^2}{R_A J}} \right) \quad (8)$$

$$\therefore \omega(t) = \frac{R_A}{\alpha^2} \left(e^{-\frac{\alpha^2 t}{R_A J}} - 1 \right) \quad (9)$$

for $t > 0$.

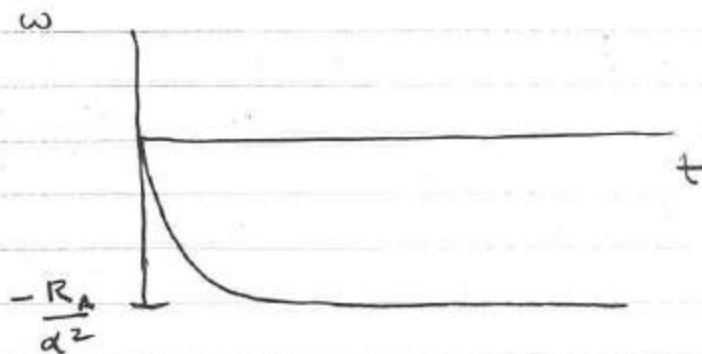

b) For steady state $\omega = -\frac{R_A}{\alpha^2}$

With the switch thrown the equation for the armature circuit becomes

$$-E_A + R_A i_A + e_m = 0$$

$$\text{or } -E_A + R_A i_A + \alpha \omega = 0 \Rightarrow i_A = -\frac{\alpha \omega + E_A}{R_A}$$

(5) becomes

$$J \dot{\omega} + \alpha \left(\frac{\alpha \omega + E_A}{R_A} \right) = -T_A$$

$$J \dot{\omega} + \frac{\alpha^2 \omega}{R_A} = -T_A + \frac{\alpha E_A}{R_A} \quad (10)$$

Can solve with either L.T. or ODE theory HW10-4.

ODE Theory. Suppose we restart our stop watch at the time we close the circuit.

$$\text{Then } \omega(0) = -\frac{R_A}{\alpha^2}$$


The solution to (10) is ($\tau_A = U(t) = 1$ for $t > 0$)

$$\omega_h = A e^{-\frac{\alpha^2 t}{R_A J}} \quad \omega_p = \left(-1 + \frac{\alpha E_A}{R_A}\right) \frac{R_A}{\alpha^2}$$

Apply I.C's $\Rightarrow$

$$A - \frac{R_A}{\alpha^2} + \frac{E_A}{\alpha} = -\frac{R_A}{\alpha^2} = A = -\frac{E_A}{\alpha}$$
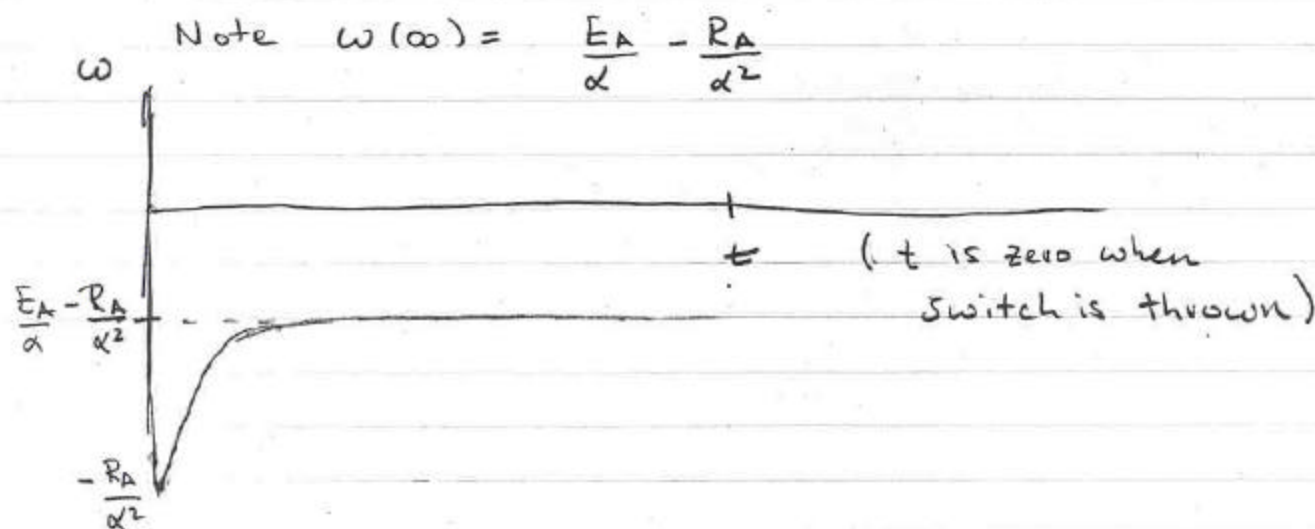
$$\therefore \omega(t) = \frac{E_A}{\alpha} \left(1 - e^{-\frac{\alpha^2 t}{R_A J}}\right) - \frac{R_A}{\alpha^2}$$



c) In this case we re-set our stop watches so that $t=0$ corresponds to when we remove the external torque. Thus, $\omega(0) = \frac{E_A}{\alpha} - \frac{R_A}{\alpha^2}$

The ODE is


$$J \dot{\omega} + \frac{\alpha^2 \omega}{R_A} = \frac{\alpha E_A}{R_A}$$

The solution is (the same as part b)

$$\omega = \omega_p + \omega_h = \frac{E_A}{\alpha} + B e^{-\frac{\alpha^2 t}{R_A J}}$$

$$\omega(0) = \frac{E_A}{\alpha} - \frac{R_A}{\alpha^2} = \frac{E_A}{\alpha} + B \Rightarrow B = -\frac{R_A}{\alpha^2}$$
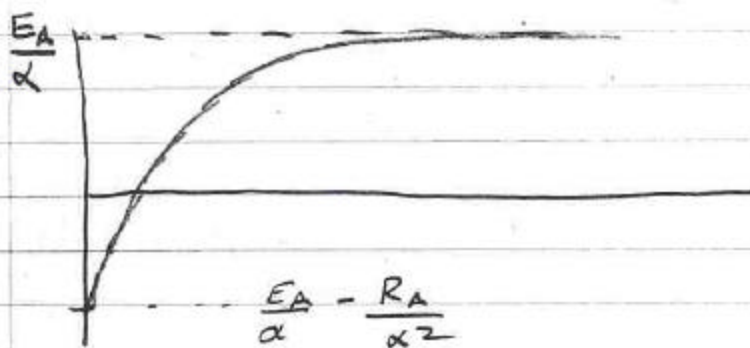
$$\therefore \omega = \frac{E_A}{\alpha} - \frac{R_A}{\alpha^2} e^{-\frac{\alpha^2 t}{R_A J}}$$



+ (t is zero when the load is removed).

- 10.21 The magnetic field of a small motor is supplied by a permanent magnet. The following two sets of measurements are made in the steady state with a 6-V battery connected across the armature. When there is no load and negligible friction, the motor rotates at 100 rad/s. When the motor is mechanically blocked to prevent its movement, the armature current is 2 A. The rotor is then attached to a propeller, which creates a viscous-friction load of $2.0 \times 10^{-3} \text{ N}\cdot\text{m}\cdot\text{s}$, and the 6-V battery is again connected across the armature. Find the steady-state speed of the propeller.

For steady state ($L \frac{di_A}{dt} = 0$), the equation

for the voltage drop in the armature $\Rightarrow$

$$-E_A + R_A i_A + \alpha \omega = 0 \quad (1)$$

and the steady state motion for the rotor

$$J \ddot{\phi} = -B\omega + i_A \omega - \tau_a = 0 \quad (2)$$

Mechanically blocked $\Rightarrow$

$$E_A = 6 \text{ V} \quad \omega = 0 \Rightarrow i_A = 2 \text{ A} \Rightarrow$$

$$-6 \text{ V} = -R_A \cdot 2 \text{ A} \Rightarrow R_A = 3 \Omega \quad (3)$$

No load, no friction

The equation of motion for the rotor is

$$J \ddot{\phi} = \tau_e = \alpha i_A \quad (4)$$

The equation for the current is

$$-E_A + R_A i_A + \alpha \omega = 0 \Rightarrow i_A = \frac{E_A - \alpha \omega}{R_A} \quad (5)$$

$$\text{So } J\dot{\omega} + \frac{\alpha^2 \omega}{R_A} = \frac{\alpha E_A}{R_A} \quad (6)$$

Implies steady state speed is ($\dot{\omega} = 0$)

$$\omega_{ss} = \frac{\alpha E_A}{R_A} \frac{R_A}{\alpha^2} = \frac{E_A}{\alpha} \quad (7)$$

$$\therefore \alpha = \frac{E_A}{\omega_{ss}} = \frac{6V}{100 \text{ rad/sec}} = 0.06 \frac{V \cdot \text{sec}}{\text{rad}} \quad (8)$$

Attach a viscous load of $B\omega$ ($B = 2 \times 10^{-3} \text{ Nm} \cdot \text{s}$)

Equation of motion (4) becomes

$$J\dot{\omega} = \tau_e - B\omega = \alpha i_A - B\omega \Rightarrow \quad (9)$$

$$J\dot{\omega} + B\omega = \alpha \left(\frac{E_A - \alpha \omega}{R_A} \right) \quad (10)$$

or

$$J\dot{\omega} + \left(B + \frac{\alpha^2}{R_A} \right) \omega = \frac{\alpha E_A}{R_A} \quad (11)$$


Steady-state $\Rightarrow (\dot{\omega} = 0)$

$$\omega_{ss} = \frac{\alpha E_A}{R_A \left(B + \frac{\alpha^2}{R_A} \right)}$$

$$\omega_{ss} = \frac{6}{100} \cdot \frac{6}{\left(\frac{2}{1000} \cdot 3 + \left(\frac{6}{100} \right)^2 \right)}$$

$$\omega_{ss} = \frac{36}{\left(\frac{6}{10} + \frac{36}{100} \right)} = \frac{36}{.96} = 37.5 \frac{\text{rad}}{\text{Sec}}$$

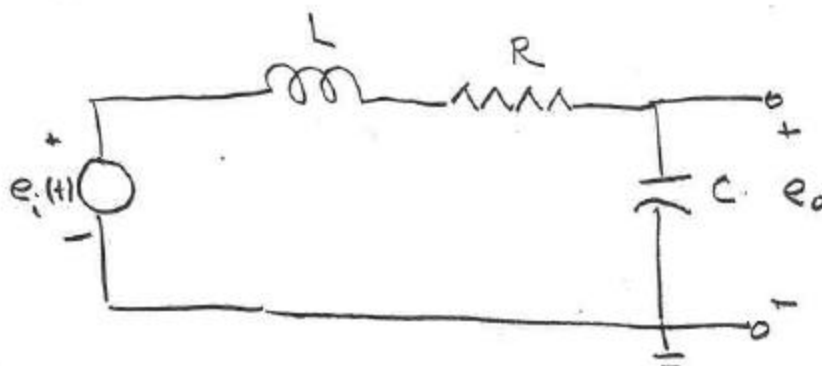1. Suppose you have the circuit shown below.
- What is its impedance?
 - What is the transfer function, i.e. the ratio $E_o(s)/E_i(s)$?
 - Suppose $L = 1$ and $C = 1$. Suppose $e_i(t) = H(t)$ where H is the Heaviside step function.
 - What does the output voltage look like as a function of time if $R = 1$?
 - What value of resistance would result in an overshoot of 10%? Plot the response as a function of time for this value of R . What is the response time t_R , i.e. the time at which $e_o(t)$ first equals 90% of its steady state value?
 - Repeat part ii for an overshoot of 2%. (The response time is the time at which it equals 98% of its steady-state value).
 - How much slower is the system's response, i.e. what is the percentage increase in the response time when the overshoot is reduced from 10% to 2%?
 - How does your answer to iv depend on the values of L or C ?



a. Impedance: elements in series $\Rightarrow$ add impedances.

$$Z = Ls + R + \frac{1}{Cs}$$

b. $I \cdot Z = E_i$

$$E_o = \frac{1}{Cs} \cdot I(s) = \frac{E_i}{Cs \cdot Z}$$

$$\frac{E_o(s)}{E_i(s)} = \frac{1}{Cs \cdot Z} = \frac{1}{LCs^2 + RCs + 1}$$

c. Given $L=1$, $C=1$. Laplace T. for output looks like

$$E_o(s) = \frac{1}{s^2 + Rs + 1} \quad E_i(s) = \frac{1}{s(s^2 + Rs + 1)}$$

This is the problem that we solved in class where use solution from class notes or use the following:

Partial Fractions

$$E_o = \frac{A}{s} + F(s)$$

$$A = \lim_{s \rightarrow 0} s E_o(s) = 1$$

$$F(s) = \frac{1}{s(s^2 + Rs + 1)} - \frac{1}{s} = \frac{1 - s^2 - Rs - 1}{s(s^2 + Rs + 1)}$$

$$= -\frac{(s+R)}{s^2 + Rs + 1}$$

Complete the square for denominator.

$$F(s) = -\frac{s+R}{\left(s + \frac{R}{2}\right)^2 + 1 - \frac{R^2}{4}} \quad \left(\text{see Table B.1} \right)$$

p 646

$$= \frac{Bs + C}{(s+a)^2 + \omega^2}$$

$$B = -1 \quad C = -R$$

$$a = \frac{R}{2} \quad \omega = \sqrt{1 - \frac{R^2}{4}}$$

$$\begin{aligned}
 e_o(t) &= 1 - e^{-\frac{R}{2}t} \left[\cos \omega t + \left(\frac{R - \frac{R}{2}}{\omega} \right) \sin \omega t \right] \\
 &= 1 - e^{-\frac{R}{2}t} \left[\cos \omega t + \frac{R/2}{\sqrt{1 - R^2/4}} \sin \omega t \right]
 \end{aligned}$$

i). See Mathcad plot of $e_o(t)$ for $R=1$.

ii). From class

$$OS = e^{-\frac{\zeta}{\sqrt{1-\zeta^2}} \cdot \pi} = .1$$

$$\Rightarrow -\frac{\zeta}{\sqrt{1-\zeta^2}} = -\frac{2.302}{\pi} \Rightarrow \frac{\zeta}{\sqrt{1-\zeta^2}} = 0.733$$

$$\Rightarrow \frac{\zeta^2}{1-\zeta^2} = (0.733)^2 = 0.537$$

$$\Rightarrow \zeta^2 = 0.537 - \zeta^2(0.537)$$

$$\Rightarrow \zeta^2 = \frac{0.537}{1 + 0.537} = 0.3495$$

$$\zeta = 0.591$$


$$\text{In this problem } \zeta = \frac{R}{2\sqrt{L \cdot \frac{1}{C}}} = \frac{R}{2} \Rightarrow R = 1.182$$

See Math Cad Plot.

Define Response

$$w(R) := \sqrt{1 - \left(\frac{R}{2}\right)^2}$$

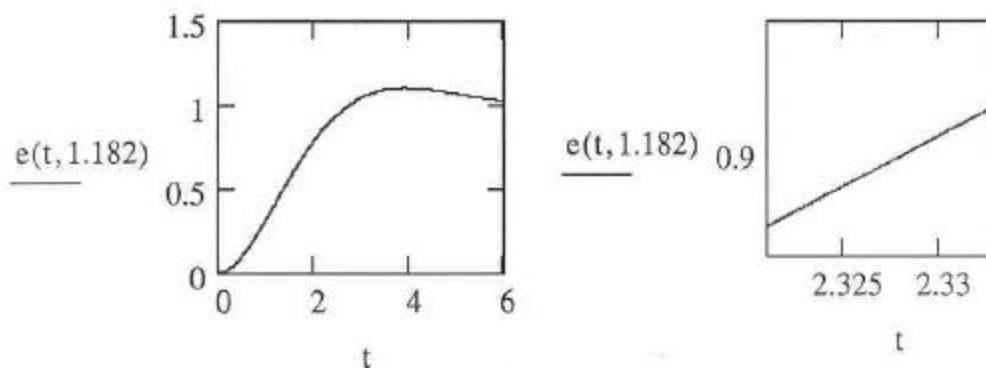
$$e(t, R) := 1 - \left(e^{-R \cdot \frac{t}{2}} \right) \cdot \left[\cos(w(R) \cdot t) + \left[\frac{R}{2 \cdot \sqrt{1 - \left(\frac{R}{2}\right)^2}} \right] \cdot \sin(w(R) \cdot t) \right]$$




Response time is approximately 2.33 seconds

Try zeta for 2 % overshoot.

Zoom in on Maximum - Note this checks

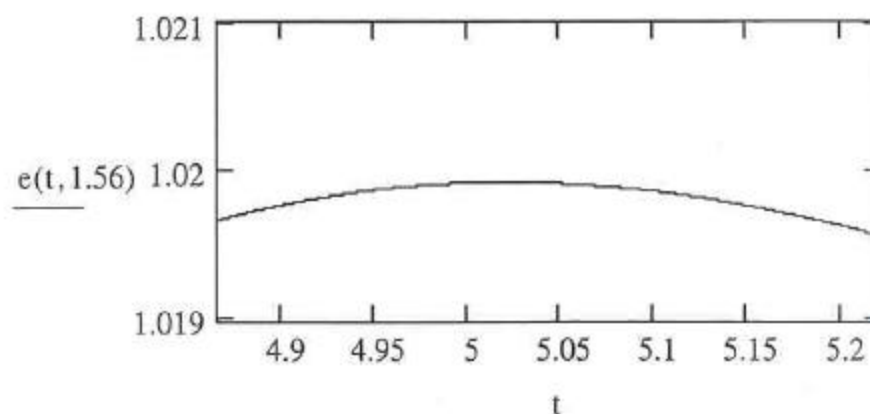

Find Response Time

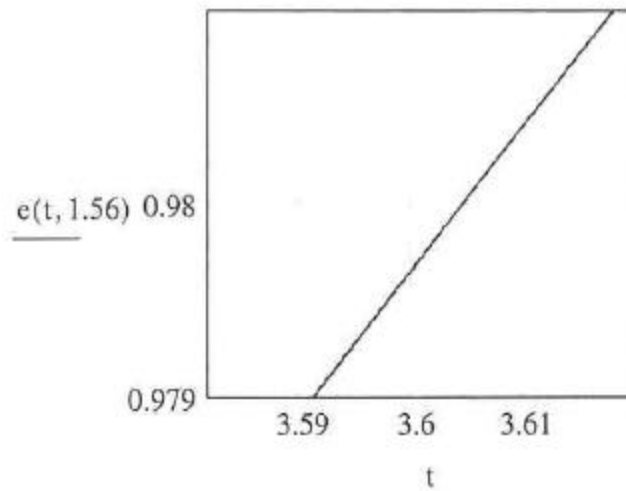

Response time is about 3.6 seconds

Percent increase is about 54% $\left(\frac{3.6 - 2.33}{2.33} \right) \cdot 100 = 54.506$