

S.1

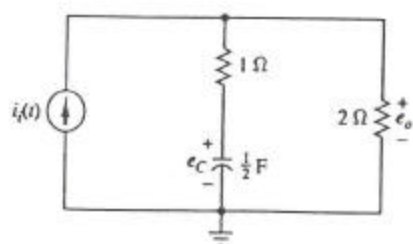



FIGURE P5.1

$$i_i = i_1 + i_2 \quad (1)$$

$$\frac{e_A - e_B}{1\Omega} = i_1 \quad (2)$$

$$i_1 = \frac{1}{2} F \cdot \frac{d(e_B - 0)}{dt} \quad (3)$$
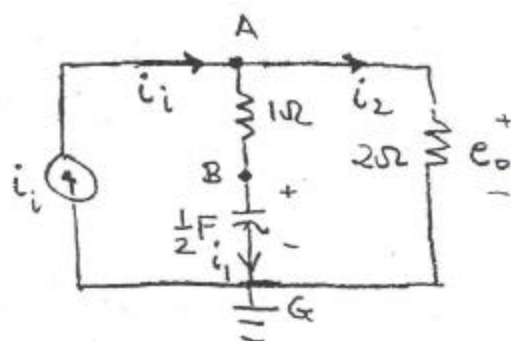
$$i_2 = \frac{e_A - 0}{2\Omega} \quad (4)$$



4 unknowns: i_1, i_2, e_A, e_B & 4 equations

This is OK at this point. # unknowns: i_1, i_2, e_A, e_B

equations: 4

Further simplification (not required)

9.7


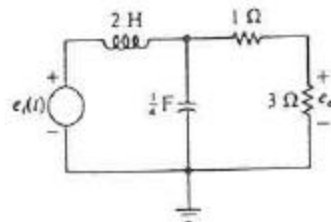


FIGURE P5.7

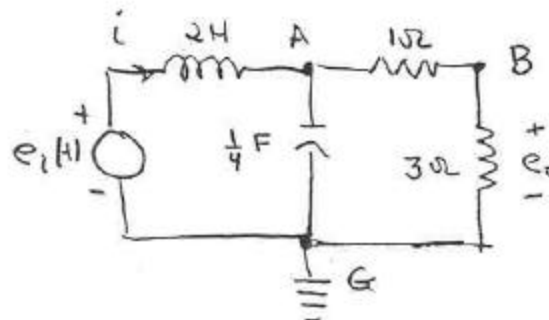

Node A:
$$i(t_0) + \frac{1}{2} \int_{t_0}^t (e_i - e_A) dt = \frac{e_A - e_B}{1} + \frac{1}{4} \dot{e}_A \quad (1)$$

Node B:
$$\frac{e_A - e_B}{1} = \frac{e_B}{3} \quad (2) \quad \text{Note } e_B = e_o$$

Node G:
$$\frac{e_B}{3} + \frac{1}{4} \dot{e}_A = i \quad (3) \quad (\text{Do not need to write this equation})$$

Unknowns: $i, e_A, e_B \quad (3)$

Equations: 3

Not Required

Note: Could simplify (2) $\Rightarrow e_A = \frac{4}{3} e_B$

Differentiate (1) & substitute

$$-\frac{1}{2} [e_i(t) - \frac{4}{3} e_B(t)] = \frac{1}{3} \dot{e}_B + \frac{1}{3} \ddot{e}_B$$

Since $e_B = e_o \Rightarrow -e_i(t) = -\frac{8}{3} e_o(t) + \frac{2}{3} \dot{e}_o + \frac{2}{3} \ddot{e}_o(t)$

5.11


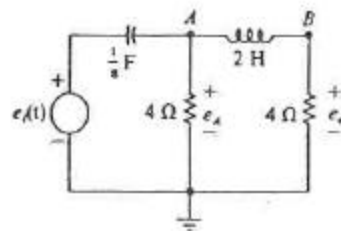


FIGURE P5.11

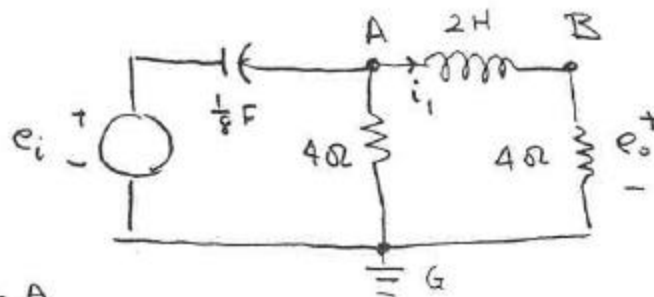

Node A:

$$\frac{1}{8} \frac{d(e_i - e_A)}{dt} = i_1(t_0) + \frac{1}{2} \int_{t_0}^t (e_A - e_B) d\tau + \frac{e_A - 0}{4} \quad (1)$$

Node B: $i_1(t_0) + \frac{1}{2} \int_0^t (e_A - e_B) d\tau = \frac{e_B}{4} \quad (2)$

Node G: $\frac{e_B}{4} + \frac{e_A}{4} = i \quad (\text{Do not need to write this equation if we are not interested in } i) \quad (3)$

Number of unknowns: e_A, e_B, i ($e_B = e_0$)

Number of equations: 3 ✓

Not Required: Simplification

(2) $\Rightarrow e_A = e_B + \frac{\dot{e}_B}{2} \quad (4)$

(1), (2) $\Rightarrow \dot{e}_i = \dot{e}_A + 2e_B + 2e_A \quad (5)$

(5), (4) $\Rightarrow \dot{e}_i = \dot{e}_B + \frac{\ddot{e}_B}{2} + 2e_B + 2(e_B + \frac{\dot{e}_B}{2})$
 $\dot{e}_i = 4e_B + 2\dot{e}_B + \frac{\ddot{e}_B}{2}$

S.12


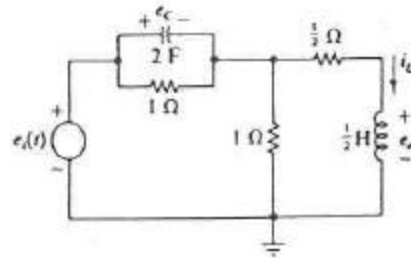


FIGURE P5.12

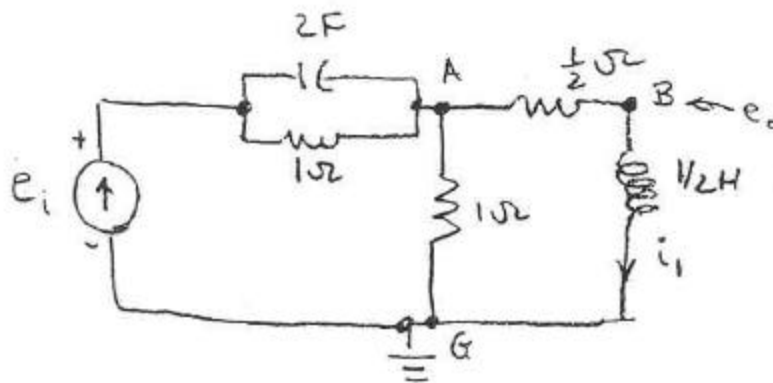

$$\text{Node A: } 2(\dot{e}_i - \dot{e}_A) + \frac{e_i - e_A}{1\Omega} = \frac{e_A - e_B}{\frac{1}{2}\Omega} + \frac{e_A}{1\Omega} \quad (1)$$

$$\text{Node B: } \frac{e_A - e_B}{\frac{1}{2}\Omega} = i_1(t_0) + \frac{1}{1/2} \int_{t_0}^t e_B(\tau) d\tau \quad (2)$$

Unknowns: e_A, e_B

of equations: 2

Not Required

$$\text{From (2) } e_A = \frac{1}{2} i_1(t_0) + \int_{t_0}^t e_B(\tau) d\tau + e_B \quad (3)$$

$$\text{or } \dot{e}_A = e_B + \dot{e}_B \quad (4)$$

$$(1) \Rightarrow 2\dot{e}_i + e_i = 2\dot{e}_A + 4e_A - 2e_B \quad (5)$$

Differentiate (5) & divide by 2. $\Rightarrow$ (use (4))

$$\ddot{e}_i + \frac{1}{2} \dot{e}_i = \dot{e}_B + \ddot{e}_B + 2(e_B + \dot{e}_B) - \dot{e}_i$$


$$\Rightarrow \ddot{e}_i + \frac{1}{2} \dot{e}_i = \ddot{e}_B + 2\dot{e}_B + 2e_B$$

where $e_B = e_o$

1. Use impedance approach.

HW 5/8

5.1

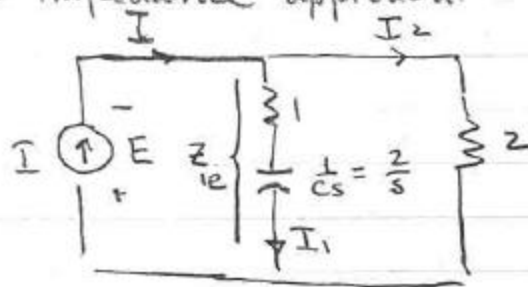


$$Z_{ie} = 1 + \frac{2}{s} = \frac{s+2}{s}$$

For two parts in parallel $Z_e = \frac{Z_{ie} \cdot 2}{2 + Z_{ie}}$

$$Z_e = \frac{\frac{s+2}{s} \cdot 2}{2 + \frac{s+2}{s}} = \frac{2s+4}{2s + s+2} = \frac{2s+4}{3s+2}$$
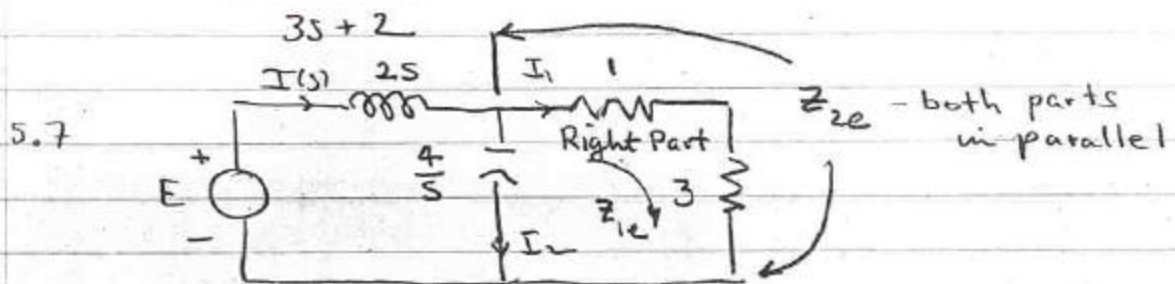
$$\therefore E(s) = \frac{2s+4}{3s+2} I(s)$$



Elements in series $\Rightarrow Z_{ie} = 4$


$$\text{Elements in parallel} \Rightarrow Z_{2e} = \frac{\frac{4}{s} \cdot 4}{4 + \frac{4}{s}} = \frac{\frac{4}{s}}{1 + \frac{1}{s}} \cdot \frac{s}{s} = \frac{4}{s+1}$$

$$Z_{\text{Total}} = Z_T = 2s + Z_{2e}$$


$$Z_T = \frac{2s(s+1) + 4}{s+1} = \frac{2s^2 + 2s + 4}{s+1} = 2 \frac{(s^2 + s + 2)}{s+1}$$

$$\therefore E(s) = \frac{2(s^2 + s + 2)}{s+1} I(s)$$

Corrected Solution

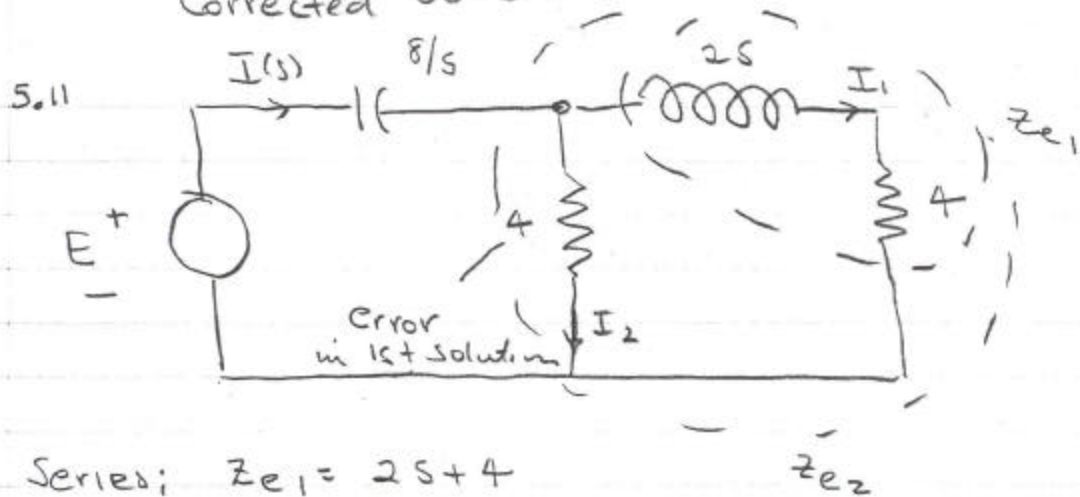

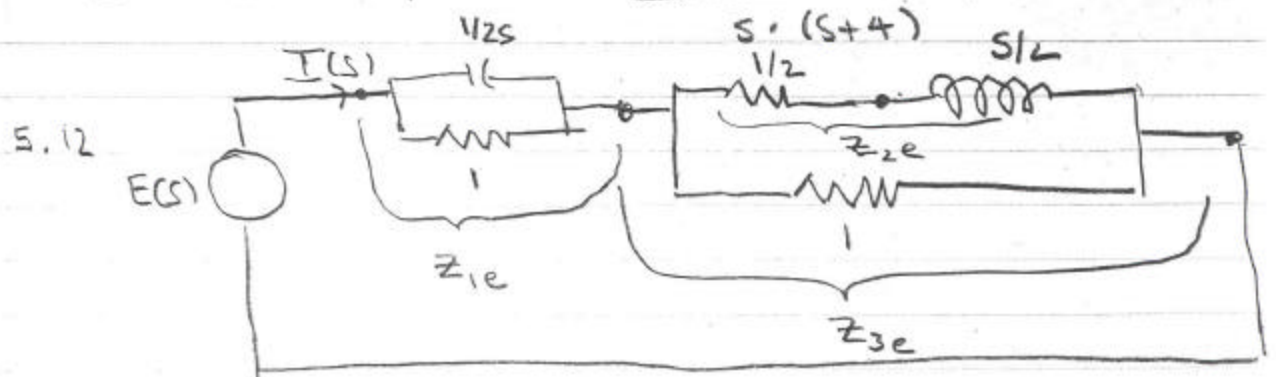Then $E(s) = Z_T I(s) = \frac{4s^2 + 16s + 32}{s(s+4)}, I(s)$



Series: $z_{e2} = \frac{1}{2} + \frac{s}{2} = \frac{1+s}{2}$


Parallel: $z_{e3} = \frac{1 \cdot z_{e2}}{1 + z_{e2}} = \frac{(1+s)/2}{1 + \frac{(1+s)}{2}} = \frac{1+s}{s+3}$

Total Impedance (Series): $z_T = z_{e1} + z_{e3}$

$$z_T = \frac{1}{1+2s} + \frac{1+s}{s+3} = \frac{s+3 + (s+1) \cdot (1+2s)}{(1+2s)(s+3)}$$

$$z_T = \frac{2s^2 + 4s + 4}{(1+2s)(s+3)}$$
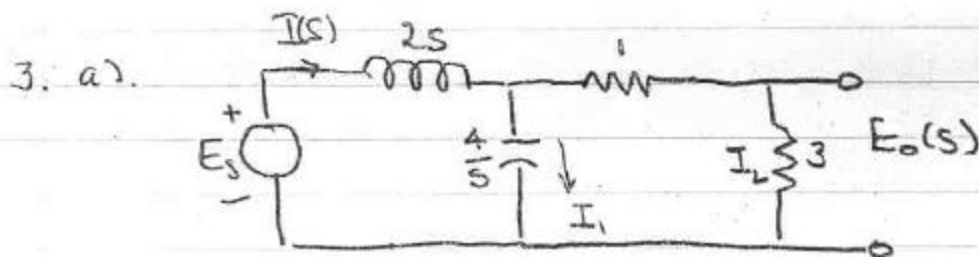
$$\therefore E(s) = \frac{2s^2 + 4s + 4}{(1+2s)(s+3)}$$



From class $I_2 = I \cdot \frac{z_1}{z_1 + z_2} = I(s) \cdot \frac{\frac{4}{s}}{4 + 4/s} = \frac{s}{s+1} I(s)$

$$\Rightarrow I_2(s) = I(s) \cdot \frac{1}{s+1}$$

$$E_o(s) = 3 \cdot I_2(s) = \frac{3}{s+1} \cdot I(s) = \frac{3}{s+1} \cdot \frac{s+1}{2(s^2+s+2)} E(s)$$

$$E_o(s) = \frac{3}{2(s^2+s+2)} \cdot E(s)$$

If $e_i(t) = 3 \cdot H(t) \xrightarrow{L.T} E(s) = \frac{3}{s}$

$\therefore E_o(s) = \frac{9}{2 \cdot s \cdot (s^2 + s + 2)}$

b). Poles

$s = 0$

$s^2 + s + 2 = 0 \Rightarrow s_j = \frac{-1 \pm \sqrt{1-8}}{2}$

$s_j = \frac{-1 \pm j\sqrt{7}}{2}$

c). Single pole at $s=0$. Other poles in Left-hand plane. Yes

Then

$e_o(\infty) = \lim_{s \rightarrow 0} s \cdot E_o(s) = \frac{s \cdot 9}{2 \cdot s \cdot (s^2 + s + 2)} \Big|_{s=0}$

$e_o(\infty) = \frac{9}{4}$