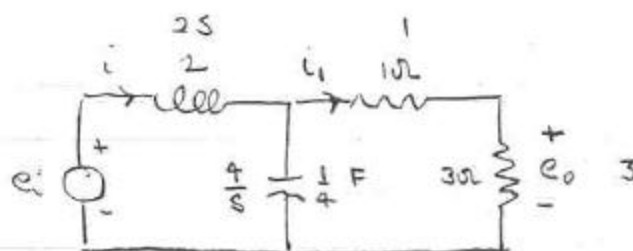


5.7



HWB-1

From last week $Z_T = \frac{2(s^2 + s + 2)}{s + 1}$ $E_i(s) = Z_T \cdot I(s)$

Current sharing rule.

$$I_1 = \frac{\frac{4}{s} I}{\frac{4}{s} + 4} = \frac{1}{1+s} I(s).$$

Output voltage $E_o(s) = 3 \cdot I_1(s) = \frac{3}{1+s} \cdot \frac{E_i(s)}{Z_T}$

$$E_o(s) = \frac{3}{1+s} \cdot \frac{s+1}{2 \cdot (s^2 + s + 2)} \cdot \frac{V_o}{s} = \frac{3}{2(s^2 + s + 2)} \cdot \frac{V_o}{s}$$

Poles $s=0$ $s^2 + s + 2 = 0 \Rightarrow s = \frac{-1 \pm \sqrt{1 - 4 \cdot 2}}{2}$

Complex roots. $s_{1,2} = -\frac{1}{2} \pm j\frac{\sqrt{7}}{2}$ $s_1 = -\frac{1}{2} + j\frac{\sqrt{7}}{2}$ $s_2 = s_1^*$
 $\ast$ - complex conjugate

$$E_o(s) = \frac{A}{s} + \frac{B}{s - s_1} + \frac{C}{s - s_2} = \frac{3V_o}{2} \frac{1}{s(s - s_1)(s - s_1^*)}$$

$$A = \frac{3V_o}{2} \frac{1}{s_1 s_1^*} = \frac{3V_o}{2 \left(\frac{1}{4} + \frac{7}{4} \right)} = \frac{3V_o}{4}$$

$$B = \frac{3V_o}{2} \cdot \frac{1}{s_1 \cdot (s_1 - s_1^*)}$$

$$C = \frac{3V_o}{2} \frac{1}{s_1^* (s_1^* - s_1)} = B^*$$

$$\therefore e_o(t) = \frac{3V_o}{4} H(t) + B e^{s_1 t} + C e^{s_1^* t} \quad \text{HW8-2}$$

$$e_o(t) = \frac{3V_o}{4} H(t) + e^{-\frac{1}{2}t} \left(B e^{j\frac{\sqrt{7}}{2}t} + B^* e^{-j\frac{\sqrt{7}}{2}t} \right)$$

$$= \frac{3}{4} V_o H(t) + e^{-\frac{t}{2}} \left((B+B^*) \cos \frac{\sqrt{7}}{2} t + (B-B^*) j \sin \frac{\sqrt{7}}{2} t \right)$$

$$B+B^* = 2 \operatorname{Re}\{B\}$$

$$B-B^* = 2j \operatorname{Im}\{B\}$$

$$\text{Consider } B: \quad B = \frac{3V_o}{2} \frac{1}{D}$$


$$\begin{aligned} D &= s_1 (s_1 - s_1^*) = \left(-\frac{1}{2} + j\frac{\sqrt{7}}{2}\right) \left[\left(-\frac{1}{2} + j\frac{\sqrt{7}}{2}\right) - \left(-\frac{1}{2} - j\frac{\sqrt{7}}{2}\right)\right] \\ &= \left(-\frac{1}{2} + j\frac{\sqrt{7}}{2}\right) j\sqrt{7} \\ &= -\frac{\sqrt{7}j}{2} - \frac{7}{2} \end{aligned}$$

$$B = \frac{3V_o}{2} \frac{1}{\frac{-7 - \sqrt{7}j}{2}} = \frac{3V_o (-7 + \sqrt{7}j)}{49 + 7}$$

$$B = 3V_o \frac{(-7 + \sqrt{7}j)}{56}$$

$$\therefore e_o(t) = \frac{3}{4} V_o \cdot H(t) + e^{-\frac{t}{2}} \left(-\frac{42}{56} V_o \cos\left(\frac{\sqrt{7}}{2}t\right) - \frac{2 \cdot 3V_o \sqrt{7}}{56} \sin\left(\frac{\sqrt{7}}{2}t\right) \right)$$
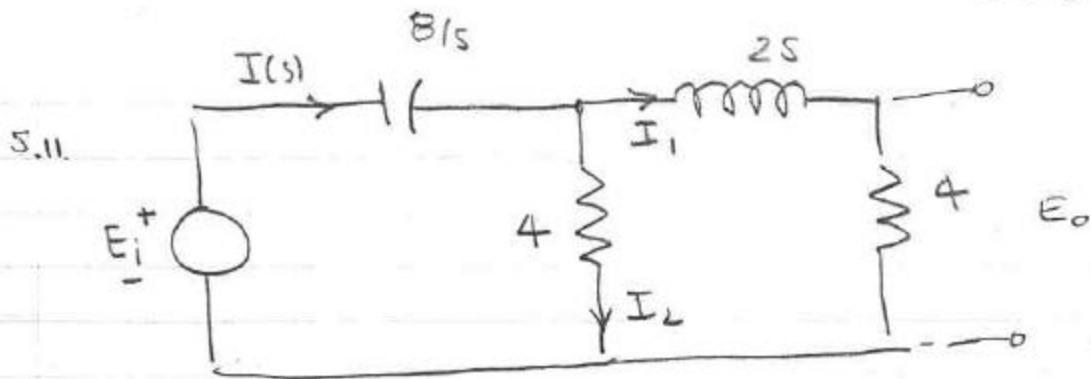
$$e_o(t) = \frac{3}{4} V_o \cdot H(t) + V_o e^{-\frac{t}{2}} \left[-\frac{3}{4} \cos\left(\frac{\sqrt{7}}{2}t\right) - \frac{3\sqrt{7}}{28} \sin\left(\frac{\sqrt{7}}{2}t\right) \right]$$



From last week

$$Z_T = \frac{4 \cdot (s^2 + 4s + 8)}{s \cdot (s + 4)}$$

$$E_i = \frac{V_o}{s} \Rightarrow I(s) = \frac{V_o}{8} \cdot \frac{8 \cdot (s + 4)}{4 \cdot (s^2 + 4s + 8)}$$

current sharing:

$$I_1(s) = \frac{4 I(s)}{2s + 8} = \frac{2}{s + 4} I(s)$$

$$E_o(s) = 4 \cdot I_1(s) = \frac{8}{s + 4} \cdot I(s) = \frac{8}{s + 4} \cdot \frac{V_o (s + 4)}{4(s^2 + 4s + 8)}$$

$$E_o(s) = \frac{2 V_o}{s^2 + 4s + 8}$$

Complete the square $s^2 + 4s + 8 = (s + 2)^2 + 4$

$$E_o(s) = V_o \left[\frac{\omega}{(s + 2)^2 + \omega^2} \right] \quad \text{where } \omega = 2.$$

$\Rightarrow$ (Tables).

$$e_o(t) = V_o e^{-2t} \sin 2t$$

Alternative Method

$$E_0(s) = \frac{A}{s} + G(s)$$

$$A = \lim_{s \rightarrow 0} s E_0(s) = \frac{3}{2 \cdot 2} = \frac{3}{4} V_0$$

$$G(s) = \frac{3V_0}{2s(s^2+s+2)} - \frac{3V_0}{4s}$$

$$= \frac{3V_0}{4} \frac{2 - (s^2+s+2)}{s(s^2+s+2)}$$

$$= \frac{3V_0}{4} \cdot \frac{-(s+1)}{s^2+s+2}$$

$$= -\frac{3V_0}{4} \frac{s+1}{(s+\frac{1}{2})^2 + \frac{7}{4}}$$

$$= -\frac{3V_0}{4} \cdot \frac{Bs+C}{(s+a)^2+\omega^2}$$


where $B=1$, $C=1$, $a=1/2$, $\omega = \frac{\sqrt{7}}{2}$

From tables

$$g(t) = e^{-t/2} \cdot \left[\cos \omega t + \frac{(1-\frac{1}{2})}{\omega} \sin \omega t \right] \left(-\frac{3}{4} \right)$$

$$\therefore e_0(t) = \frac{3V_0}{4} H(t) - \frac{3V_0}{4} e^{-\frac{t}{2}} \left[\cos \omega t + \frac{1}{2\omega} \sin \omega t \right] \checkmark$$

$$\omega = \frac{\sqrt{7}}{2}$$

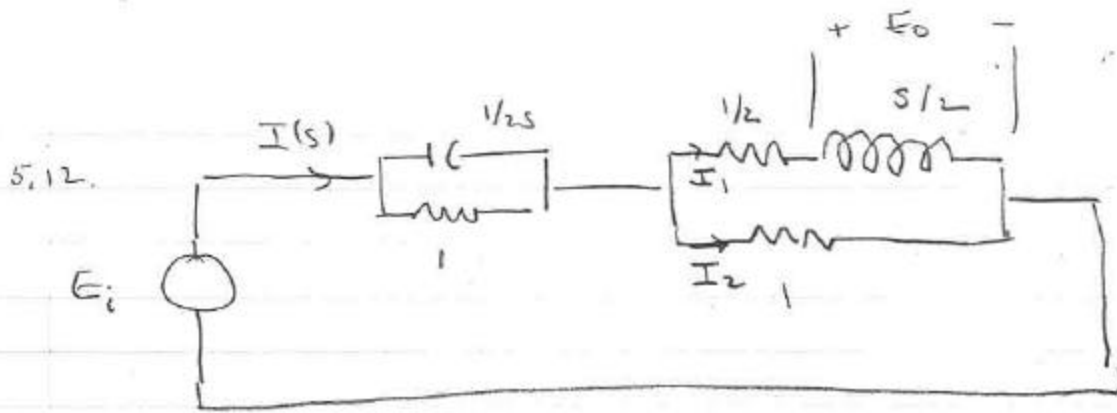

From last week

$$E_i(s) = \frac{2s^2 + 4s + 4}{(1+2s)(s+3)} I(s)$$

Current sharing

$$I_1 = \frac{1}{1 + 1/2 + \frac{s}{2}} I(s) = \frac{2}{s+3} I(s)$$

$$I_1(s) = \frac{2}{s+3} \cdot \frac{(1+2s)(s+3)}{2(s^2+2s+2)} E_i(s)$$

$$= \frac{1+2s}{s^2+2s+2} \frac{V_0}{s}$$


$$E_o = \frac{s}{2} I_1(s) = \frac{V_0}{2} \cdot \frac{1+2s}{s^2+2s+2}$$

Complete the square $s^2+2s+2 = (s+1)^2+1$

$$E_o(s) = \frac{V_0}{2} \frac{2s+2-1}{(s+1)^2+1} = V_0 \frac{(s+1)}{(s+1)^2+1} - \frac{V_0}{2} \frac{1}{(s+1)^2+1}$$

$$e_o(t) = V_0 \cdot e^{-t} \left[\cos t - \frac{1}{2} \sin t \right]$$

5, 34

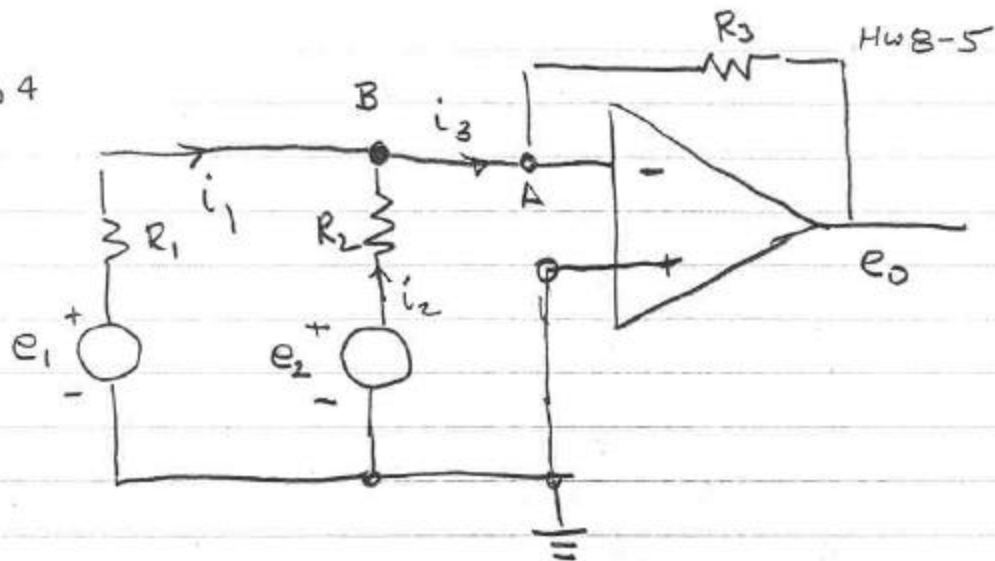

Approximations

- No current flow through op-amp
- $e_A \approx 0$

Sum currents at node B.


$$i_1 + i_2 = i_3$$

$$e_A \approx 0 \Rightarrow i_1 = \frac{e_1}{R_1} \quad i_2 = \frac{e_2}{R_2} \quad i_3 = -\frac{e_0}{R_3}$$


$$\therefore \frac{e_1}{R_1} + \frac{e_2}{R_2} = -\frac{e_0}{R_3}$$

$$\text{or } e_0 = -\frac{R_3}{R_1} e_1 - \frac{R_3}{R_2} e_2$$

5.37

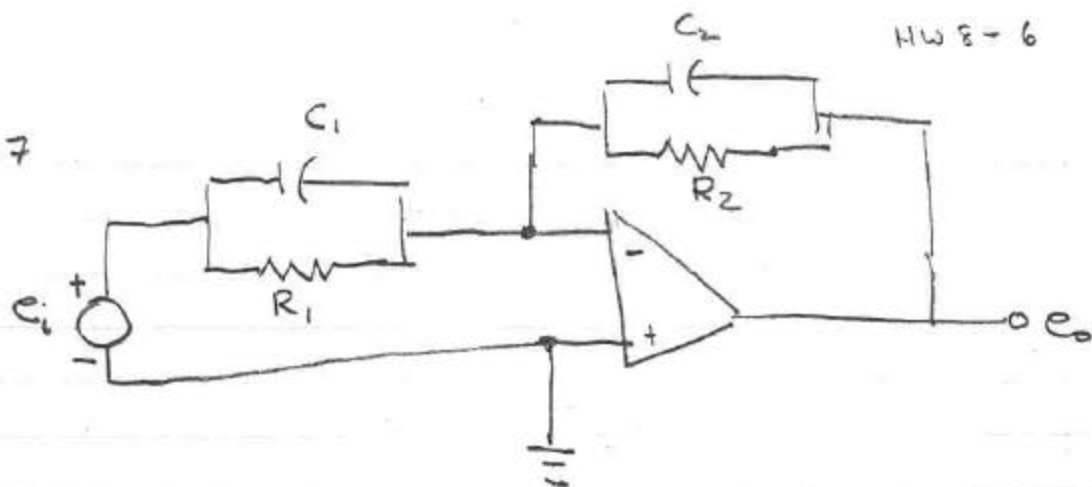

Take Laplace Transform

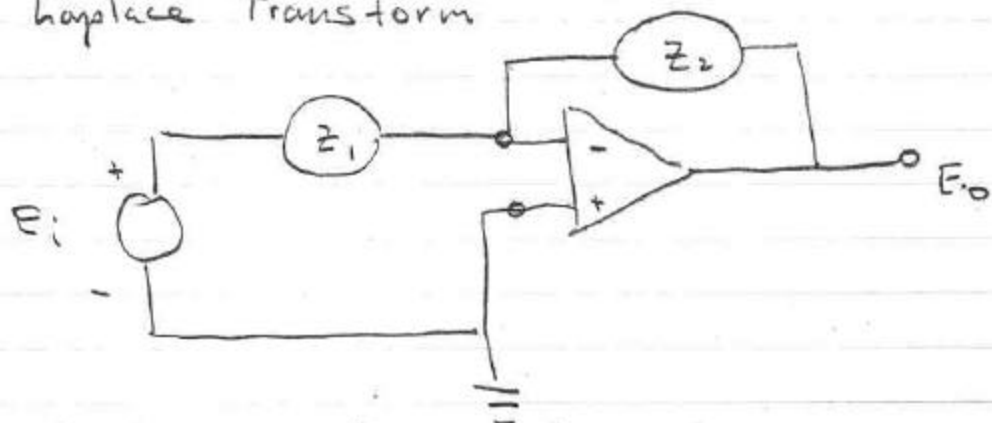Same situation as discussed in class $\Rightarrow$

$$E_o(s) = - \frac{Z_2}{Z_1} E_i(s)$$

$$Z_2 = \frac{R_2 \cdot \frac{1}{C_2 s}}{R_2 + \frac{1}{C_2 s}} = \frac{R_2}{R_2 C_2 s + 1}$$

Similarly

$$Z_1 = \frac{R_1}{R_1 C_1 s + 1} \Rightarrow E_o(s) = - \frac{R_2}{R_1} \frac{R_1 C_1 s + 1}{R_2 C_2 s + 1}$$

$$\text{or } (R_1 R_2 C_2 s + R_1) E_o(s) = - (R_2 R_1 C_1 s + R_2) E_i(s)$$

$$\Rightarrow R_1 R_2 C_2 \frac{de_o}{dt} + R_1 e_o(t) = - \left(R_2 R_1 C_1 \frac{de_i}{dt} + R_2 e_i(t) \right)$$