

- 5.16 a) Explain why the rules for series and parallel resistors cannot be used for the circuit shown in Figure P5.16.
b) Use the node-equation method to find the voltages of nodes A and B with respect to the ground node.
c) Find the currents i_o and i_1 and the equivalent resistance connected across the source.

61.

Current Equation for node A

$$\frac{10 - e_A}{10} = \frac{e_A - e_B}{10} + \frac{e_A - 0}{5} \quad (1)$$

C) Find i_0 and i_1 and the equivalent resistance.

Note $i_1 = i_2 + i_3$

$$i_2 = \frac{10 - e_A}{10} = 1 - \frac{e_A}{10} = 1 - \frac{40}{110}$$

$$i_3 = \frac{10 - e_B}{10} = 1 - \frac{50}{110}$$

$$i_1 = i_2 + i_3 = 1 - \frac{40}{110} + 1 - \frac{50}{110} = 2 - \frac{90}{110} = 1 \frac{2}{11} = \frac{13}{11}$$

$$i_0 = \frac{e_B - e_A}{10} = \frac{\frac{50}{11} - \frac{40}{11}}{10} = \frac{10}{10 \cdot 11} = \frac{1}{11}$$

Equivalent Resistance

$$10V = R_e \cdot i_1 \Rightarrow R_e = \frac{10}{\frac{13}{11}} = \frac{110}{13}$$

8.34 Find the transfer function for the circuit shown in Figure 8.12 by characterizing the passive elements by their impedances.

$$Z_{e1} = \frac{1}{3s} + 2s \quad (\text{series})$$

$$= \frac{1 + 6s^2}{3s}$$

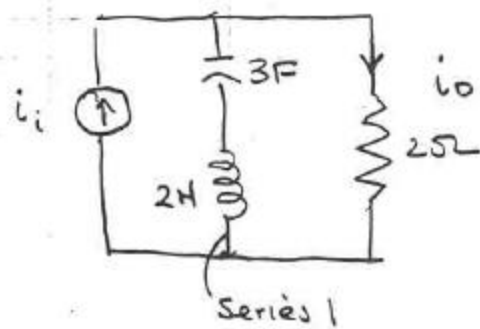


Fig 8.12

Current sharing rule:

$$I_0(s) = I_i(s) \cdot \frac{Z_{e1}}{Z_{e1} + 2} = I_i(s) \cdot \frac{1 + 6s^2}{3s} \cdot \frac{1}{\left(\frac{1 + 6s^2}{3s} + 2\right)}$$


$$= I_i(s) \cdot \frac{1 + 6s^2}{6s^2 + 6s + 1} \quad T(s) = \frac{1 + 6s^2}{6s^2 + 6s + 1}$$

- 8.39 a) Use impedances and the results of Example 8.16 to find the transfer function for the op-amp circuit shown in Figure P8.39.
b) Plot the pole-zero pattern.

HW 9-3

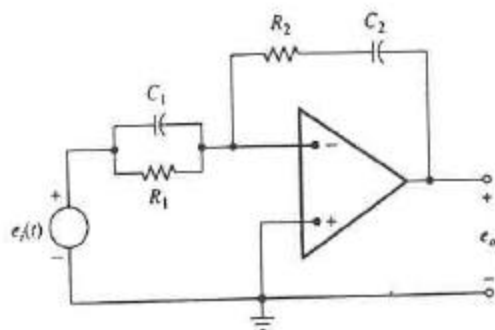(a) From Example 8.16.

$$\frac{E_o(s)}{E_i(s)} = - \frac{Z_2(s)}{Z_1(s)}$$



Z_1 : Elements in parallel.

$$\Rightarrow Z_1 = \frac{\frac{R_1}{C_1 s}}{\frac{1}{C_1 s} + R_1} = \frac{R_1}{1 + R_1 C_1 s}$$

Z_2 : Elements in series

$$Z_2 = R_2 + \frac{1}{C_2 s} = \frac{R_2 C_2 s + 1}{C_2 s}$$

$$\begin{aligned} \text{Then } \frac{E_o(s)}{E_i(s)} &= - \frac{R_2 C_2 s + 1}{\frac{C_2 s \cdot R_1}{1 + R_1 C_1 s}} \\ &= - \frac{(R_2 C_2 s + 1)(R_1 C_1 s + 1)}{C_2 s R_1} \end{aligned}$$

$$\frac{E_o(s)}{E_i(s)} = - \frac{(R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_2 C_2) s + 1)}{C_2 s R_1} = T(s).$$

Grader:

This step

not necessary.

$$= - \left(R_2 C_1 s + \frac{(R_1 C_1 + R_2 C_2)}{C_2 R_1} + \frac{1}{C_2 R_1 s} \right)$$

Takes derivative

Gain


Integrates.

ADDITIONAL PROBLEMS

1. See problem sheet.


Note $\boxed{A}$ - additive op-amp $\boxed{G}$ - linear gain op-amp $\boxed{D}$ - op-amp takes derivative

See handout for actual configuration

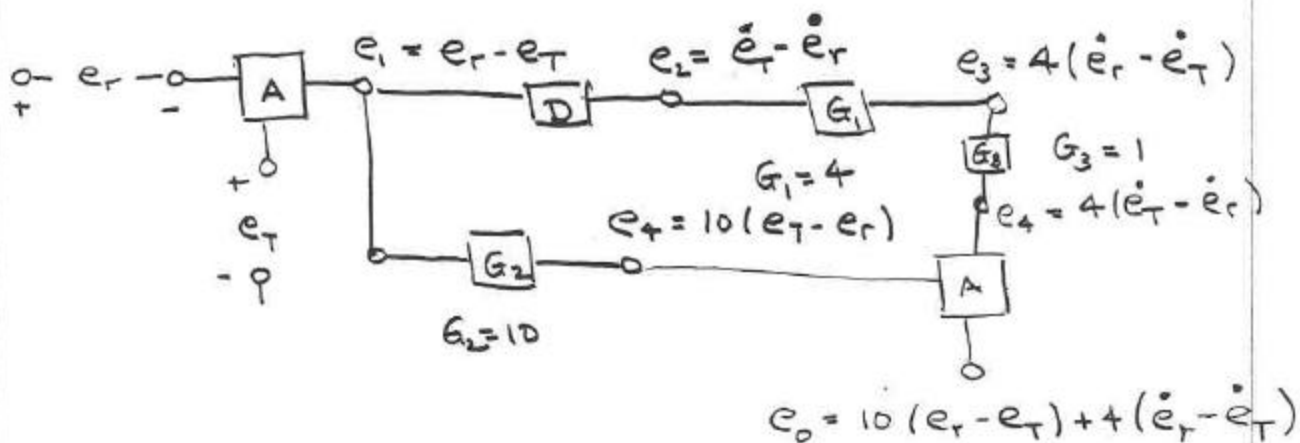

2. Need an op-amp configuration that will integrate.

We know that

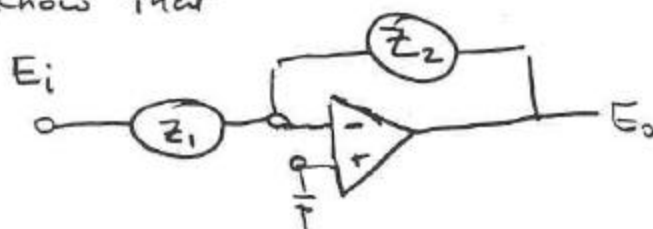

$$E_o = -\frac{Z_2}{Z_1} E_i$$


Integration: want $-\frac{Z_2}{Z_1} = -\frac{3}{s} \Rightarrow Z_2 = 3$
 $Z_1 = s$

$$\Rightarrow Z_2 = 3\Omega \text{ (Resistor)}$$


$$Z_1 = s \text{ (inductor)}$$

(could use capacitor for Z_2 and resistor for Z_1)

i.e. Op-Amp looks like

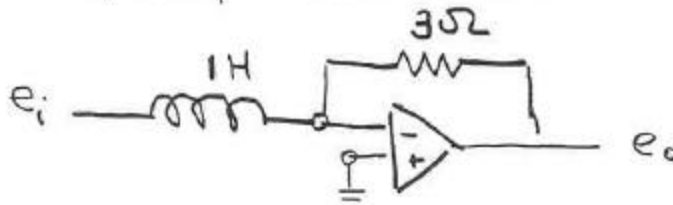

Alternatively it could look like.

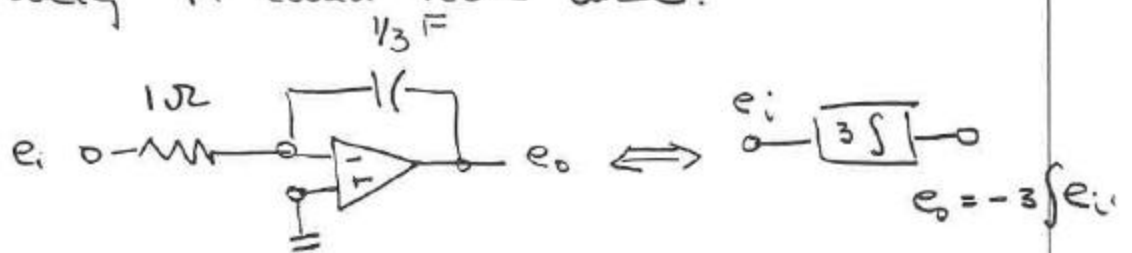

Then full circuit

