

24-352 Dynamic Systems and Control: MAKE-UP QUIZ #1

Close book and notes. You have 30 minutes to complete the following questions.


NAME: _____

19 February 2001

The current $i(t)$ in the electric circuit shown in the figure satisfies the following differential equation

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = \dot{e}_1(t)$$

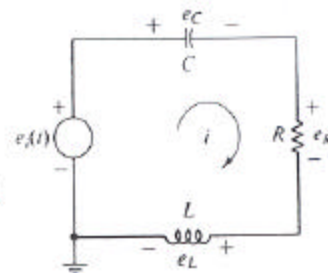where $L = 1$, $R = 0.1$, and $C = 0.01$, and the input voltage $e_1(t) = E_0 \sin(\omega t)$.
Find the steady-state current $i(t)$ in the circuit.



ANSWER

Solution

1) 1st Approach

$$e_i = E_0 e^{j\omega t} \checkmark$$

3 { Solve for z where $L \ddot{z} + R \dot{z} + \frac{1}{C} z = j\omega E_0 e^{j\omega t} \checkmark$

$i = \text{Im} \{z\} \checkmark$

2) 2nd approach

$$e_i = E_0 \sin \omega t \Rightarrow \dot{e}_i = \omega E_0 \cos \omega t$$

Assume $\dot{e}_i = \omega E_0 e^{j\omega t}$

$$L \ddot{z} + R \dot{z} + \frac{1}{C} z = \omega E_0 e^{j\omega t}$$

Then $i = \text{Re} \{z\}$

Either way gives same solution.

$$z = A e^{j\omega t}$$

1st Approach. $\Rightarrow \left[\left(\frac{1}{C} - L\omega^2 \right) + jR\omega \right] A e^{j\omega t} = j\omega E_0 e^{j\omega t} \checkmark$


(2) $A = \frac{j\omega E_0}{\left(\frac{1}{C} - L\omega^2 \right) + jR\omega} \checkmark$

Express $A = \frac{R_1 e^{j\phi_1}}{R_2 e^{j\phi_2}} \checkmark$

$R_1 = \omega E_0 \checkmark \quad \phi_1 = \frac{\pi}{2} \checkmark$

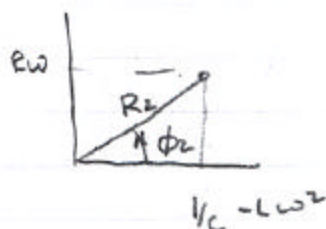(5) $R_2 = \sqrt{\left(\frac{1}{C} - L\omega^2 \right)^2 + R^2 \omega^2} \checkmark$

$\phi_2 = \tan^{-1} \left(\frac{R\omega}{\frac{1}{C} - L\omega^2} \right) \checkmark$



$$\text{Then } Z = \frac{R_1}{R_2} e^{j(\omega t + \phi_1 - \phi_2)} \quad \checkmark$$

(2)

$$\therefore i(t) = \frac{\omega E_0 \sin(\omega t + \overset{\phi_1}{\frac{\pi}{2}} - \phi_2)}{\sqrt{(\frac{1}{C} - L\omega^2)^2 + R^2\omega^2}} \quad \checkmark$$

$$\text{Since } \sin(x + \frac{\pi}{2}) = \cos x \Rightarrow$$

$$i(t) = \frac{\omega E_0 \cos(\omega t - \phi_2)}{\sqrt{(\frac{1}{C} - L\omega^2)^2 + R^2\omega^2}}$$

For the values given $L=1$, $R=0.1$ and $C=.01$

$$i(t) = \frac{\omega E_0 \cos(\omega t - \phi_2)}{\sqrt{(100 - \omega^2)^2 + 0.01\omega^2}} \cos(\omega t - \phi_2) \quad \left\{ \text{or } \sin(\omega t + \frac{\pi}{2} - \phi_2) \right\}$$

where

$$\phi_2 = \tan^{-1} \left(\frac{R\omega}{\frac{1}{C} - L\omega^2} \right) = \tan^{-1} \left(\frac{0.1\omega}{100 - \omega^2} \right)$$