

Total  
Points = 11.

11

## 24-352 Dynamic Systems and Control: QUIZ 4

Close book and notes. You have 45 minutes to complete the following questions.

NAME: Solutions


12 March 2001

Consider the circuit shown in Figure 1. Assume that  $L = 3$ ,  $C = 1/6$ , and  $R = 2$ .

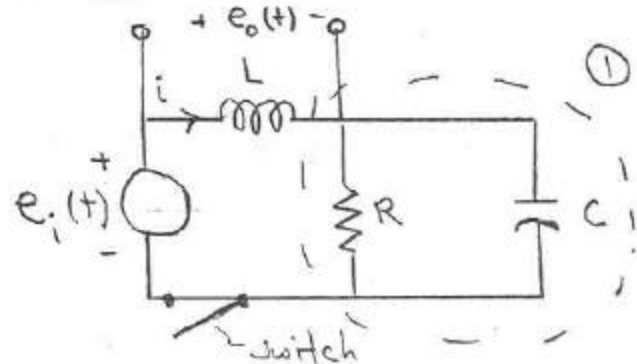1. Find the circuit's impedance.
2. Assume that the circuit has zero initial values. What is the Laplace transform of the total current flowing through the circuit,  $I(s)$ , in terms of the Laplace transform of the input voltage  $E_i(s)$ ?
3. Suppose that the voltage source is a 3 Volt DC battery. At  $t = 0$ , an open switch in the circuit is closed so that the 3 Volts is suddenly applied to the circuit. Use your impedance and Laplace transform theory to determine the output voltage as a function of time,  $t$ .

ANSWER

$$Z_{le} = \frac{R \cdot \frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{R}{RCs + 1}$$



$$(4) \quad Z_T = Ls + Z_{le} \Rightarrow$$

$$Z_T = \frac{Ls(RCs + 1) + R}{RCs + 1} = \frac{LCRs^2 + Ls + R}{RCs + 1}$$

Substitute values of parameters  $\Rightarrow$

$$Z_T = \frac{s^2 + 3s + 2}{\frac{1}{3}s + 1}$$

Figure 1

$f(t)$	$F(s)$
$H(t)$	$1/s$
$e^{-at}$	$\frac{1}{s+a}$

$$(1) \quad I(s) = \frac{E_i(s)}{Z_T} = \frac{\frac{1}{3}s + 1}{s^2 + 3s + 2} \cdot E_i(s)$$

$$3. \quad E_o(s) = L \cdot s \cdot I(s) = \frac{3s \left( \frac{1}{3}s + 1 \right)}{s^2 + 3s + 2} \cdot \frac{3}{s} = \frac{3s + 9}{s^2 + 3s + 2}$$

$$\text{But } s^2 + 3s + 2 = (s+1)(s+2)$$

$$(6) \quad E_o(s) = \frac{3s + 9}{(s+1)(s+2)} = \frac{A}{s+1} + \frac{B}{s+2} \quad (\text{partial fractions})$$

Multiply by  $s+1$  & set  $s = -1 \Rightarrow$

$$A = \frac{3(-1)+9}{1} = 6 \quad \checkmark$$

Multiply by  $s+2$  & set  $s = -2 \Rightarrow$

$$B = \frac{3(-2)+9}{(-2+1)} = -3 \quad \checkmark$$

$$\therefore E_0(s) = \frac{6}{s+1} - \frac{3}{s+2}$$

From tables  $e_0(t) = 6e^{-t} - 3e^{-2t} \quad \checkmark$