

Quiz 6 SOLUTIONS

1. An electric motor.

- (3) (a) Armature circuit ✓
 (b) Circuit for electro magnet ✓
 (c) Armature and shaft ✓
- Note to grader - students may use similar terms.

2. Circuit (a):

$$e_a(t) = i_a R_A + e_m = i_a R_A + \alpha \omega \quad (1)$$

(4) Armature (c):

$$J\dot{\omega} = -B\omega - \tau_L + \tau_e = -B\omega - \tau_L + \alpha i_a \quad (2)$$

(Note: can write $e_m = \alpha \omega$ and $\tau_e = \alpha i_a$ as separate equations)

3. Laplace Transforms (1) $\Rightarrow$

$$E_a(s) = I_a R_A + \alpha \Omega(s) \quad \text{or} \quad I_a = \frac{E_a - \alpha \Omega}{R_A} \quad (3)$$

(2) & (3) $\Rightarrow$ ($\tau_L = 0$)

$$J s \Omega(s) + B \Omega(s) = \alpha I_a = \frac{\alpha E_a - \alpha^2 \Omega}{R_A} \quad (4)$$

(4)

$$\therefore \left(J s + B + \frac{\alpha^2}{R_A} \right) \Omega(s) = \frac{\alpha E_a(s)}{R_A}$$

$$\text{or} \quad \Omega(s) = \frac{\alpha E_a(s)}{R_A \left(J s + B + \frac{\alpha^2}{R_A} \right)}$$

$$T(s) = \frac{\alpha}{R_A \left(J s + B + \frac{\alpha^2}{R_A} \right)} \quad (5)$$

2.

$$4. \quad e_a(t) = E_0 H(t) \Rightarrow E_a(s) = \frac{E_0}{s} \quad \checkmark$$

$$U(s) = \frac{\alpha E_0}{R_A s (Js + B + \frac{\alpha^2}{R_A})} = \frac{A}{s} + \frac{B}{\left(s + B + \frac{\alpha^2}{R_A}\right)} \quad \checkmark$$

$$A = \lim_{s \rightarrow 0} s \cdot U(s) = \frac{\alpha E_0}{R_A (B + \frac{\alpha^2}{R_A})} \quad \checkmark$$

$$(7) \quad B = \lim_{s \rightarrow -\frac{B + \alpha^2/R_A}{J}} \left(s + \frac{B + \alpha^2/R_A}{J} \right) U(s) = \frac{\alpha E_0}{J R_A \left(-\frac{B + \alpha^2/R_A}{J} \right)} \quad \checkmark$$

$$\therefore U(s) = \frac{\alpha E_0}{R_A (B + \frac{\alpha^2}{R_A})} \left(\frac{1}{s} - \frac{1}{s + 1/\tau} \right) \quad \checkmark$$

$$\text{where } \tau = J / (B + \frac{\alpha^2}{R_A}) \quad \checkmark$$

$$\therefore w(t) = \frac{\alpha E_0}{R_A (B + \frac{\alpha^2}{R_A})} \cdot \left[1 - e^{-t/\tau} \right] \quad \checkmark$$

alternately, $H(t)$ may be used instead of 1.

$$(1) \quad 5. \quad \tau = \frac{J}{B + \frac{\alpha^2}{R_A}} \quad \checkmark$$

Also, they may have left $\tau = J (B + \frac{\alpha^2}{R_A})$

(1) 6. Acceptable answers: Tachometer or generator. ✓

Solution for Commonly Occurring Error.

2. Equation (2) is incorrectly written

$$J\ddot{\omega} = -B\dot{\omega} - \tau_L - \tau_e = -B\dot{\omega} - \tau_L - \alpha i_A \quad (2e)$$

Grader: -1 for writing 2e rather than (2).

3. Equation (4) becomes

$$Js^2\Omega + Bs\Omega = \alpha I_A = \frac{\alpha E_A - \alpha^2\Omega}{R_A} \quad (4e)$$

$$(4) \Rightarrow \left(Js^2 + Bs + \frac{\alpha^2}{R_A} \right) \Omega(s) = \frac{\alpha E_A(s)}{R_A}$$

$$\Rightarrow \frac{\Omega(s)}{E_A(s)} = \frac{\alpha}{R_A} \cdot \frac{1}{\left(Js^2 + Bs + \frac{\alpha^2}{R_A} \right)} \quad (5e)$$

4. Attempt to find inverse transform.

$$\text{Find poles} \quad s = \frac{-B \pm \sqrt{B^2 - 4J\frac{\alpha^2}{R_A}}}{2J} = s_1, s_2$$

$$E_A(s) = \frac{E_0}{s}$$

$\Rightarrow$

$$\Omega(s) = \frac{\alpha E_0}{J R_A s (s - s_1)(s - s_2)}$$

$$= \frac{A}{s} + \frac{B}{s - s_1} + \frac{C}{s - s_2} \quad (\text{Partial Fractions})$$

Graders: Please give partial credit for taking a shot at the inverse transform.

Solution for COE

2.

$$A = \frac{\alpha E_0}{J R_A s_1 \cdot s_2}$$

$$(7) \quad B = \frac{\alpha E_0}{J R_A s_1 \cdot (s_1 - s_2)}$$

$$C = \frac{\alpha E_0}{J R_A s_2 (s_2 - s_1)}$$

$$\text{Then } w(t) = \frac{\alpha E_0}{J R_A} \left(\frac{1}{s_1 s_2} + \frac{e^{s_1 t}}{s_1 (s_1 - s_2)} + \frac{e^{s_2 t}}{s_2 (s_2 - s_1)} \right)$$

5. There are two time constants

$$(11) \quad \tau_1 = -\frac{1}{s_1} \quad , \quad \tau_2 = -\frac{1}{s_2}$$