

Student Name_____

18-100 Introduction to Electrical and Computer Engineering, Fall 2021

Exam 2

(Total of 5 Problems)

October 26th, 2021

Note:

- 1. This exam is closed-book (a two-sided 8.5 in x 11 in note sheet is allowed)***
- 2. It has to be your own work and please show your work.***
- 3. Please remember to write units for your answers wherever is needed.***
- 4. Please box your final answers***

Student Name_____

Student Name_____

Score

Problem 1_____ (20 pts.)

Problem 2_____ (20 pts.)

Problem 3_____ (20 pts.)

Problem 4_____ (20 pts.)


Problem 5_____ (20 pts.)

Total_____ (100 pts)

Student Name_____

Student Name_____

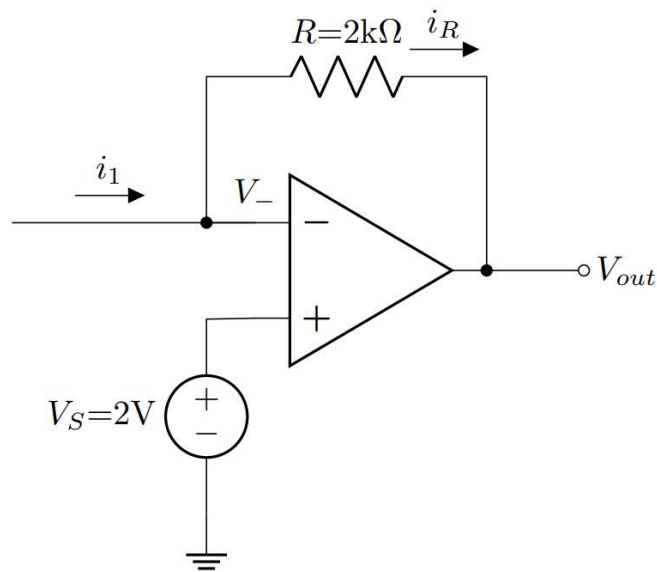- a) (20 pts) Current-to-Voltage Converter:** Consider the circuit shown in the figure below (assume that the op amp is supplied by $\pm 9\text{V}$).



For parts **a)**, **b)**, and **c)** below, assume that $i_1 = 1\text{ mA}$ and find:

- a)** (2 pts) the current i_R
- b)** (2 pts) V_- , the voltage at the “-” input terminal of the op amp
- c)** (4 pts) the voltage V_{out}

For parts **d)** and **e)** below, assume that $i_1 = -1\text{ mA}$, and find:

- d)** (4 pts) the current i_R
- e)** (4 pts) the voltage V_{out}

For part **f)** below find


- f)** (4 pts) the value of i_1 that would result in $V_{out} = -9\text{ V}$

Student Name_____

Problem 1 Solution:

Student Name_____

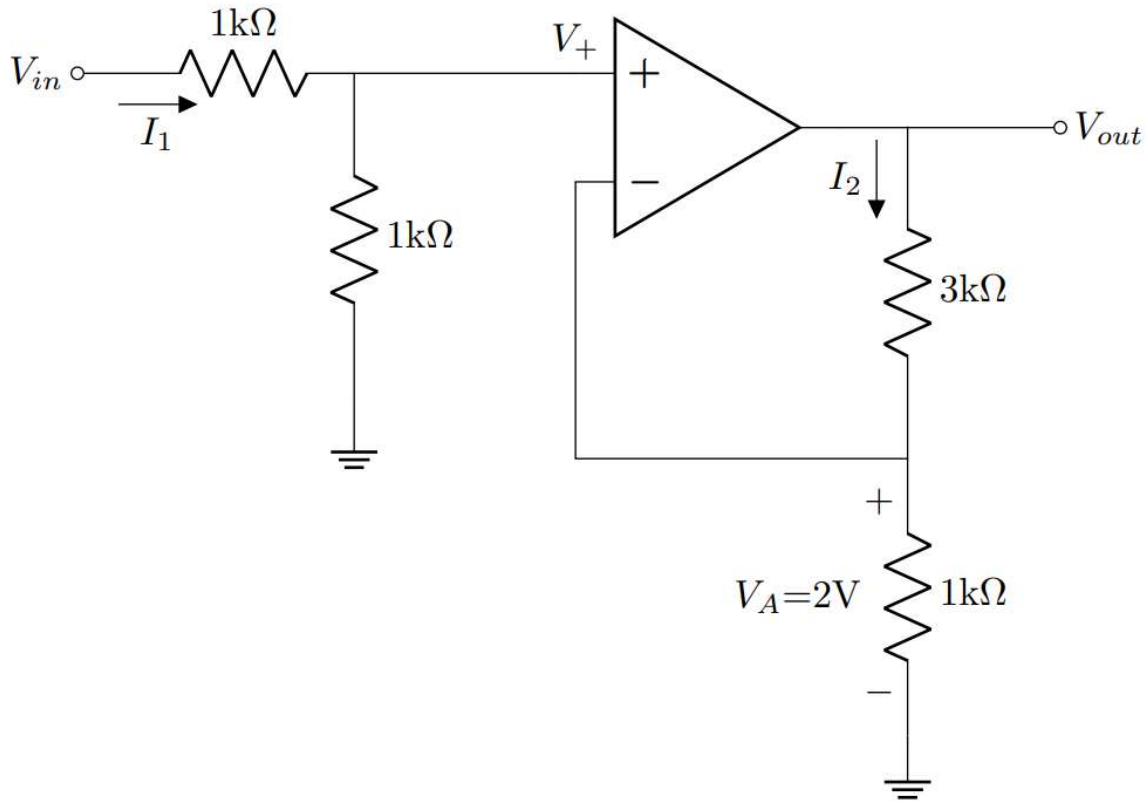2. (20 points) **Op Amp:** Consider this circuit below. Assume that the op amp is supplied by $\pm 9V$. Note that $V_A = 2V$ is labelled across one of the resistors.



Please calculate

- a) (4 pts) the current I_2
- b) (4 pts) the voltage V_{out}
- c) (4 pts) the voltage V_+
- d) (4 pts) the current I_1
- e) (4 pts) the voltage V_{in}

Student Name_____

Problem 2 Solution:

Student Name_____

(Blank page for extra work if needed – please do not write solutions here)


Student Name _____

3. (20 pts) **Quiz Questions:** For the following 5 problems, please make only one choice for each problem.

a) (4 pts) The gain of an amplifier is +40 dB. If an input signal has a peak-to-peak voltage of 1 mV, what is the peak-to-peak voltage of the output signal going to be?

- ☐ 10 mV
- ☐ 40 mV
- ☐ 100 mV
- ☐ 400 mV

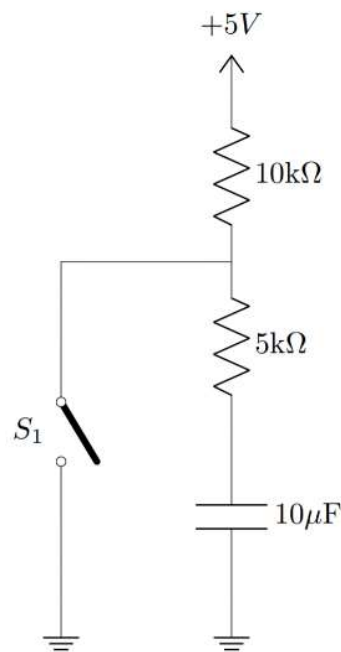b) (4 pts) In this circuit, S_1 has been open for a very long time. Approximately how long will it take the capacitor to fully *discharge* when S_1 closes?




- ☐ 167 ms
- ☐ 250 ms
- ☐ 750 ms

Student Name_____

Problem 3 Extra space for work (if needed)

Student Name _____

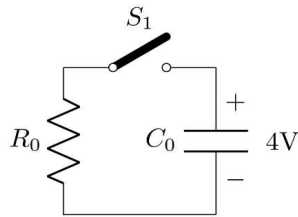- c) (4 pts) A capacitor with capacitance C_0 is charged to 4V in the diagram below. After S_1 is closed, the capacitor is allowed to discharge completely. What is the energy dissipated by R_0 during the discharge of the capacitor?




- ☐ $16C_0$ (J)
 - ☐ $8C_0$ (J)
 - ☐ $4C_0$ (J)
- d) (4 pts) The signal $v_{in}(t)$ was applied to the input of a first-order *lowpass* filter and the signal $v_{out}(t)$ was measured at the output. What is the filter's cutoff frequency?

$$v_{in}(t) = 5 \cos(10^5 t) \text{ (V)}$$

$$v_{out}(t) = 0.005 \cos\left(10^5 t - \frac{\pi}{2}\right) \text{ (V)}$$

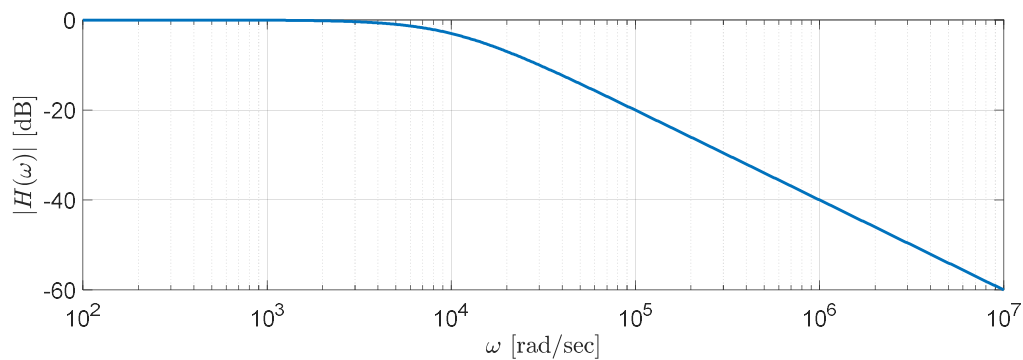
- ☐ $\omega_c = 10^2$ rad/sec
 - ☐ $\omega_c = 10^3$ rad/sec
 - ☐ $\omega_c = 10^4$ rad/sec
- e) (4 pts) The magnitude of the frequency response of a lowpass filter is plotted below. What is this filter's cutoff frequency?



- ☐ $\omega_c = 10^3$ rad/sec
- ☐ $\omega_c = 10^4$ rad/sec
- ☐ $\omega_c = 10^5$ rad/sec

Student Name_____

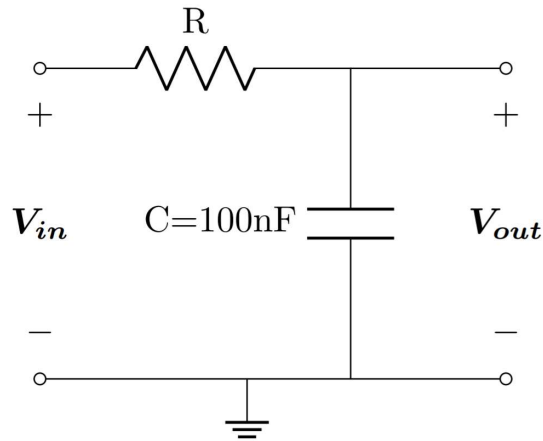4. (20 pts) **Filter:** Your small group TA gives you the lowpass RC filter pictured below, and you use Scopy to measure a cutoff frequency of $\omega_c = 10^4$ radians/second.



- a) (4 pts) If $C = 100\text{ nF}$, what is the value of the resistor R in this filter?
- b) (4 pts) What is the complex impedance of the capacitor (i.e., what is Z_c) at the cutoff frequency of $\omega_c = 10^4$ radians/second?

If an input voltage to this filter has the following form:

$$v_{in}(t) = 4 \cos(10^3 t) + 4 \cos(2 \times 10^6 t) \text{ (V)}$$

Then the output voltage has the following form:

$$v_{out}(t) = A_1 \cos(10^3 t + \phi_1) + A_2 \cos(2 \times 10^6 t + \phi_2) \text{ (V)}$$

- c) (4 pts) Determine the amplitude A_1 and show your work.
- d) (4 pts) Determine the amplitude A_2 and show your work.
- e) (4 pts) How would you change the value of R in the filter to reduce (attenuate) A_2 by an additional -20 dB? What would A_1 be if R is changed to this value?

Student Name_____



Problem 4 Solution

Student Name _____

5. (20 points) The circuit below shows a square-wave source voltage connected in series with a resistor and an inductor. The square-wave source voltage, also plotted below, has a period of 10ms and an amplitude of 5V, i.e. at $t=0$, voltage changes instantaneously from 0V to 5V and at $t=5\text{ms}$, voltage changes instantaneously from 5V back to 0V, so on and so forth. The source voltage is zero for all $t < 0$.

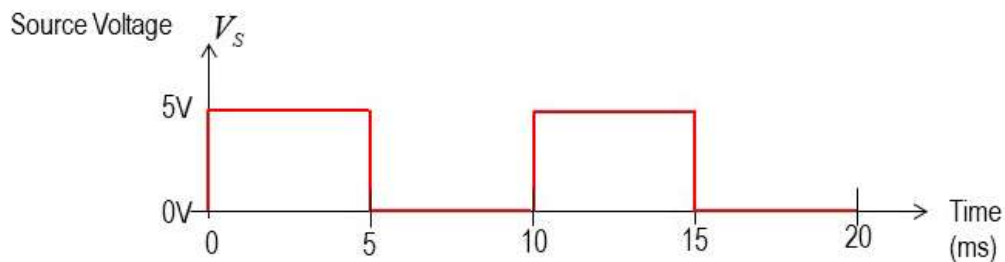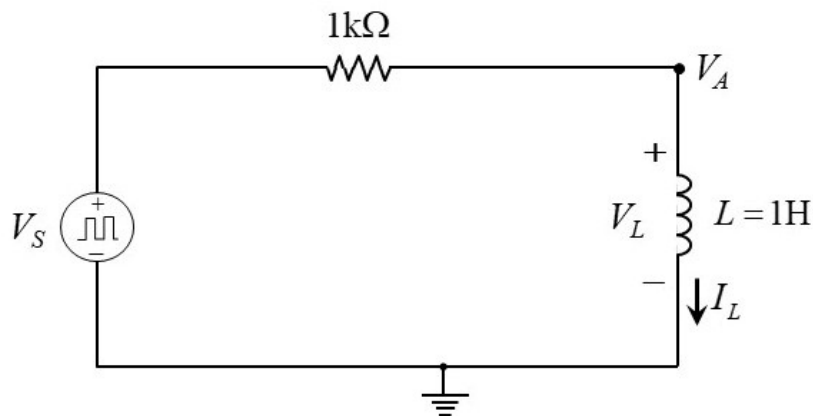- a) (4 pts) What is the inductor current I_L , as labeled in the figure, at $t=0^+$, right after the source voltage changes from 0V to 5V? What is the voltage V_A at the same instance?
- b) (4 pts) Calculate the inductor current, I_L , and the voltage V_A , both at $t=1\text{ ms}$.
- c) (4 pts) What is the inductor current I_L , at $t=5^+$ ms, right after the source voltage changes from 5V to 0V? What is the voltage V_A at the same instance?
- d) (4 pts) Calculate the inductor current, I_L , and the voltage V_A , both at $t=6\text{ ms}$.
- e) (4 pts) Using the axes drawn on the last page of this test, sketch the current I_L and voltage V_A as function of time from $t=0$ to $t=20\text{ ms}$.

(Note: V_A is measured with respect to ground and is also the voltage across the inductor, V_L , as labeled in the figure below. Also note: $1\text{ms} = 10^{-3}$ second).



Student Name_____

Problem 5 Solution

(Continue on Next Page)

Student Name _____

