

## ***18-100 Introduction to Electrical and Computer Engineering***

---

### ***Lecture 04***

## ***Binary Numbers, Boolean Logic, and Logic Gates***

# Today's Digital World: "0" and "1"

## Binary Number

### Digital music

"10011011110001...1000100010...0100101111001..."




### Data Center



**Everything is stored as**

"100...11011110001...1000100010...01001011110"

### Communications


 


**Everything is transmitted as** "100...11011110001...1000100010...01001011110"

## Quiz

1. The first general purpose computer, ENIAC, was built at Univ. of Pennsylvania in 1946 and was in operation until 1956. It contains 20,000 vacuum tubes. It used 10-digit decimal numbers for computation. Can you guess what is the clock speed of ENIAC?



- ☐ 3.5 GHz
- ☐ 25 kHz.
- ☐ 50 Hz.

  

## Quiz

  1. The first general purpose computer, ENIAC, was built at Univ. of Pennsylvania in 1946 and was in operation until 1956. It contains 20,000 vacuum tubes. It used 10-digit decimal numbers for computation. Can you guess what is the clock speed of ENIAC?

- ☐ 3.5 GHz *Intel CORE i7 Microprocessor.*
- ☒ 25 kHz.
- ☐ 50 Hz. *Frequency of ac power from wall outlet.*




## ***Learning Objectives for This Lecture***

---


- ***Why today's computer using binary numbers.***
- ***What is Boolean logic and what are logic gates.***
- ***How to use logic gates to build logic functions.***
- ***How computer uses binary numbers to control “things”.***
- ***How computer uses logic gates to do “computation”.***




## "1" and "0" : Inside a Microprocessor

 

8.5 billion transistors

 


# The Logic Levels Used Here

 

Logic Value	Logic Value	Logic Value	Voltage Value
0	False	LOW	0 (V)
1	True	HIGH	5 (V)

## Why “1” and “0”

 

***Black (“0”) and White (“1”)***  
**No Gray**

***Ensure No Mistakes: It is not so easy to “confuse” black and “white”***




## Why “1” and “0”

## Resilient to Noise

1.0	0.3	0.8	0.0	0.6	0.3
0.1	0.8	0.3	0.8	0.1	1.0
0.8	0.1	1.0	0.2	0.8	0.1
0.0	0.8	0.0	0.8	0.2	0.8
0.8	0.3	1.0	0.2	0.8	0.3
0.1	0.7	0.1	0.8	0.0	0.8



Threshold = 0.5

 


1	0	1	0	1	0
0	1	0	1	0	1
1	0	1	0	1	0
0	1	0	1	0	1
1	0	1	0	1	0
0	1	0	1	0	1

**Ensure No Mistakes: It is not so easy to “confuse” black and “white”**

## Binary Minimize the Impact of Noise

  


# Decimal Number System

 

$$d = a_{n-1} \times 10^{n-1} + a_{n-2} \times 10^{n-2} + \dots + a_1 \times 10^1 + a_0 \times 10^0$$

$$\begin{aligned}
 1982 & \quad \rightarrow \quad 1 \times 10^3 + 9 \times 10^2 + 8 \times 10^1 + 2 \times 10^0 \\
 & \quad = 1000 + 900 + 80 + 2 = 1982
 \end{aligned}$$

## Binary Number System

 


A  $n$ -bit binary number has  $2^n$  number of possible values, ranging from 0 to  $2^n - 1$

**Conversion to decimal:**  $d = a_{n-1} \times 2^{n-1} + a_{n-2} \times 2^{n-2} + \dots + a_1 \times 2^1 + a_0 \times 2^0$

$$10101011 \quad \rightarrow \quad 1 \times 2^7 + 1 \times 2^5 + 1 \times 2^3 + 1 \times 2^1 + 1 \times 2^0$$

$$= 128 + 32 + 8 + 2 + 1 = 171$$

# Decimal to Binary

 

139

$$= 2 \times 69 + 1$$

$$= 2 \times (2 \times 34 + 1) + 1$$

$$= 2 \times (2 \times 2 \times 17 + 1) + 1$$

$$= 2^3 \times (2 \times 8 + 1) + 2 + 1$$

$$= 2^7 + 2^3 + 2 + 1$$

$$= 1 \times 2^7 + 0 \times 2^6 + 0 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$$


**139**

*Decimal*

Each digit will only have two values  $\begin{cases} 1 \\ 0 \end{cases}$  (bit)

# Decimal to Binary

**13**  
Decimal

 

13

$$= 2 \times 6 + 1$$

$$= 2 \times 2 \times 3 + 1$$

$$= 2 \times 2 \times (2 + 1) + 1$$

$$= 2^3 + 2^2 + 1$$

$$= 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1$$



# Addition

Decimal  $139 + 13 =$

Binary  $10001011 + 1101 = 10011000$

$$\begin{array}{r}
 \phantom{+} 10001011 \\
 + \phantom{000} 1101 \\
 \hline
 10011000
 \end{array}$$

carry

↑↑

binary operation

## Binary to Decimal

Decimal  $139 + 13 = 152$

Binary  $10001011 + 1101 = 10011000$

Digit number

7 6 5 4 3 2 1 0  
10011000  
↑    ↑↑

$$2^7 + 2^4 + 2^3 = 128 + 16 + 8 = 152$$

10011000  
Most significant bit (MSB) ————— Least significant bit (LSB)

# Negative Number 8-bit Number

# Two's Complement

Negative Number:  $x + (-x) = 0$

Take any 8-bit binary number: 0 1 1 0 1 0 1 1  
 ↓ ↓ ↓ ↓ ↓ ↓ ↓ ↓  
 bit-wise complement: 1 0 0 1 0 1 0 0

Add the above two numbers:

	0 1 1 0 1 0 1 1	
+	1 0 0 1 0 1 0 0	bit-wise complement:
<hr/>		
	1 1 1 1 1 1 1 1	
Add 1:	+ 0 0 0 0 0 0 0 1	
<hr/>		
	1 0 0 0 0 0 0 0	$x + (-x) = 0$
	8-bit	

If  $x = 01101011$   $-x = 10010101$

↑ bit-wise-complement + 1 (2's Complement)



## Binary Number System

*2-bit binary number*

Binary	Decimal
00	0
01	1
10	2
11	3

$4 = 2^2$  values

*3-bit binary number*

Binary	Decimal
000	0
001	1
010	2
011	3
100	4
101	5
110	6
111	7

$8 = 2^3$  values

*4-bit binary number*

Binary	Decimal
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	10
1011	11
1100	12
1101	13
1110	14
1111	15

$16 = 2^4$  values

## Hexadecimal Number

A Hexadecimal number is a base 16 number: Each digit has 16 values:

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F

10 11 12 13 14 15

16 values

### Hexadecimal to Decimal

Hex		Decimal
2E	=	$2 \times 16^1 + 14 \times 16^0 = 46$

### Hexadecimal to Binary

2 E

0010 1110

Each bit in Hex is 4 bit in Binary!

0x — The number to follow is hexadecimal.

0x2E = 46


0x21 = 33

Hex	Decimal
0x2E	46
0x21	33


 
# Taking More Digits

$$\boxed{a_{n-1}} \boxed{a_{n-2}} \quad \dots \quad \boxed{a_1} \boxed{a_0}$$




## Binary to Represent Analog

$$a_{n-1} \ a_{n-2}$$

...

$$a_1 \ a_0$$

 




## A Simple Truth of “1” and “0”

*Each transistor only controls a “1” and a “0”, however,*

*8,500,000,000 Transistors can carry out very complex functions!*



# Binary Logic:

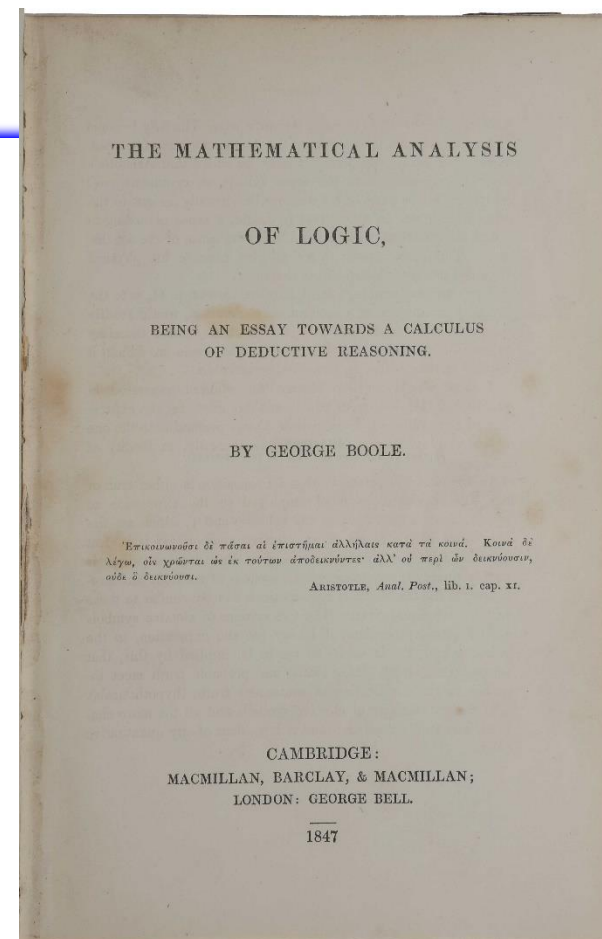
 
 


"True" = "1"

"False" = "0"

Binary bit operation: Simplest decision making






## NOT Gate: Inverter

   

Truth Table  $P = \bar{A}$

Input	Output
1	0
0	1

# AND Gate

     

## Truth Table


$$P = A \cdot B$$

Input A	Input B	Output P
0	0	0
1	0	0
0	1	0
1	1	1


$$\left\{ \begin{array}{l} 0 \cdot 0 = 0 \\ 1 \cdot 0 = 0 \\ 0 \cdot 1 = 0 \\ 1 \cdot 1 = 1 \end{array} \right.$$



 
## Using Logic Gates to Control Action: The Use of “1” and “0”



 
## Using Logic Gates to Control Action: The Use of “1” and “0”



 
## Using Logic Gates to Control Action: The Use of “1” and “0”


 
## Using Logic Gates to Control Action: The Use of “1” and “0”



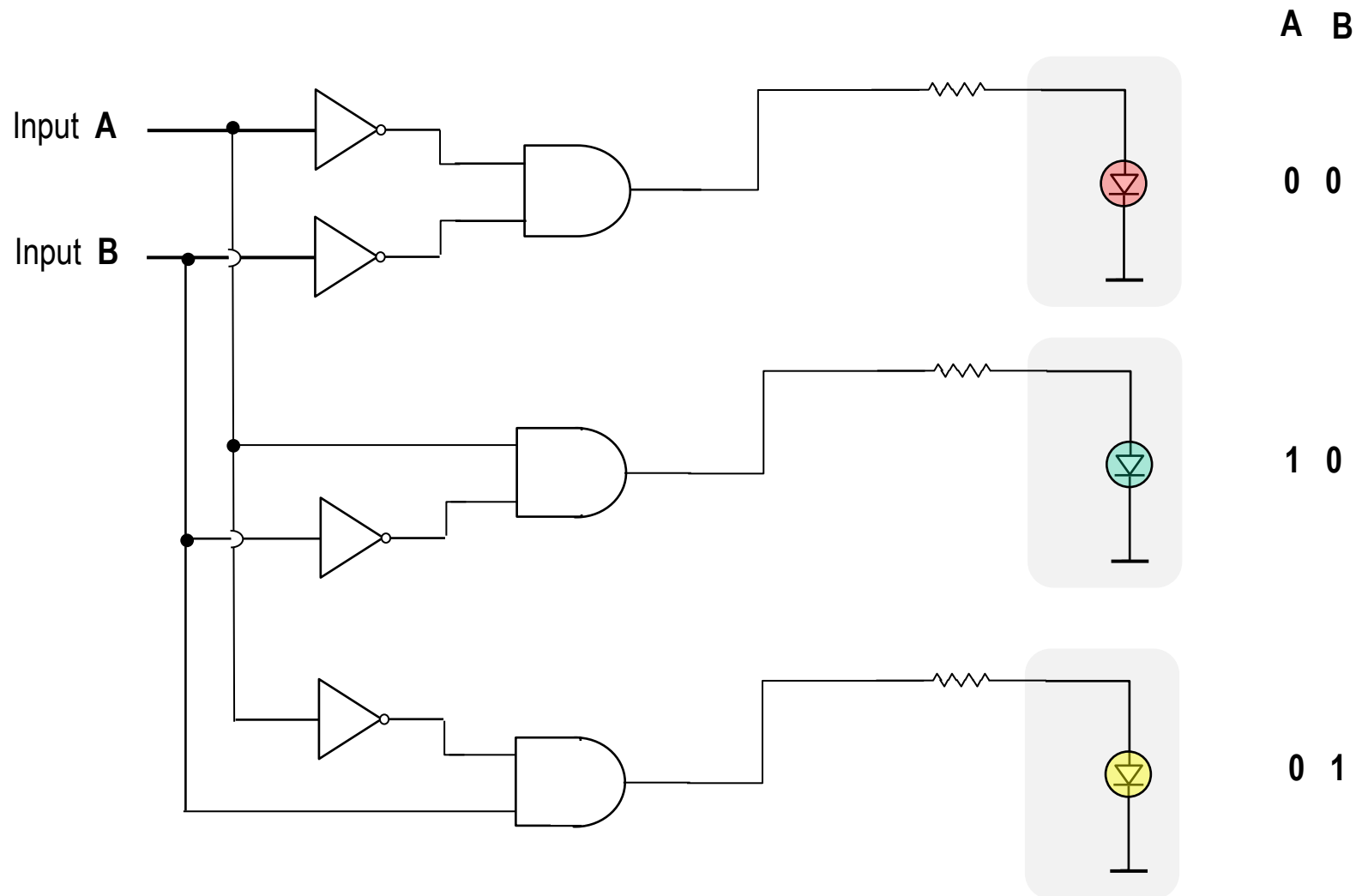
# Using Logic Gates to Control Action: The Use of "1" and "0"



## ***n-bit Input Controlling/Selecting $2^n$ Different Actions***

*A  $n$ -bit number has  $2^n$  different values: Can be used to control  $2^n$  different actions!*

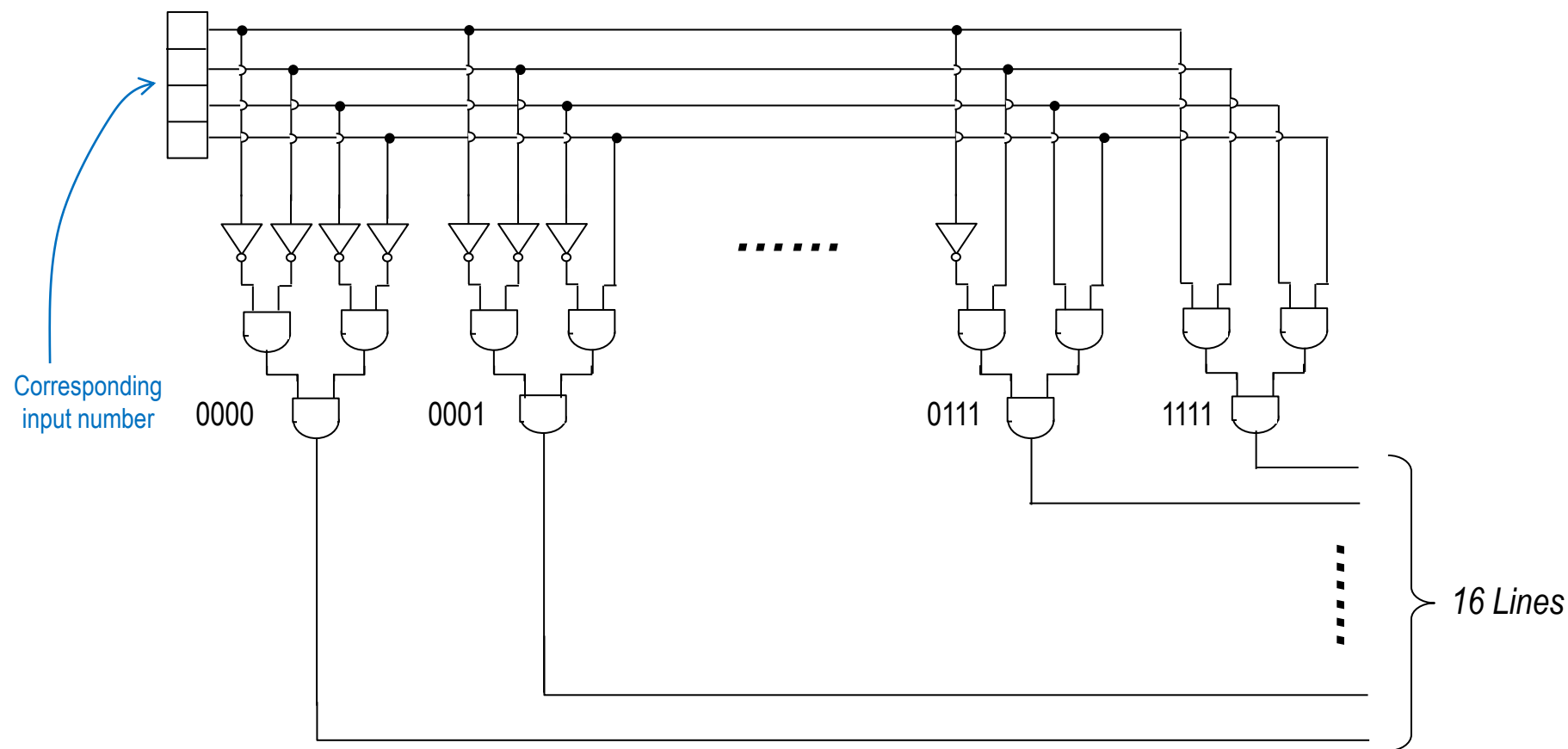*Example: 4-bit number controlling/selecting 16 lines*






## ***n-bit Input Controlling/Selecting $2^n$ Different Actions***

### ***4-bit Decode***

*4-bit binary number*

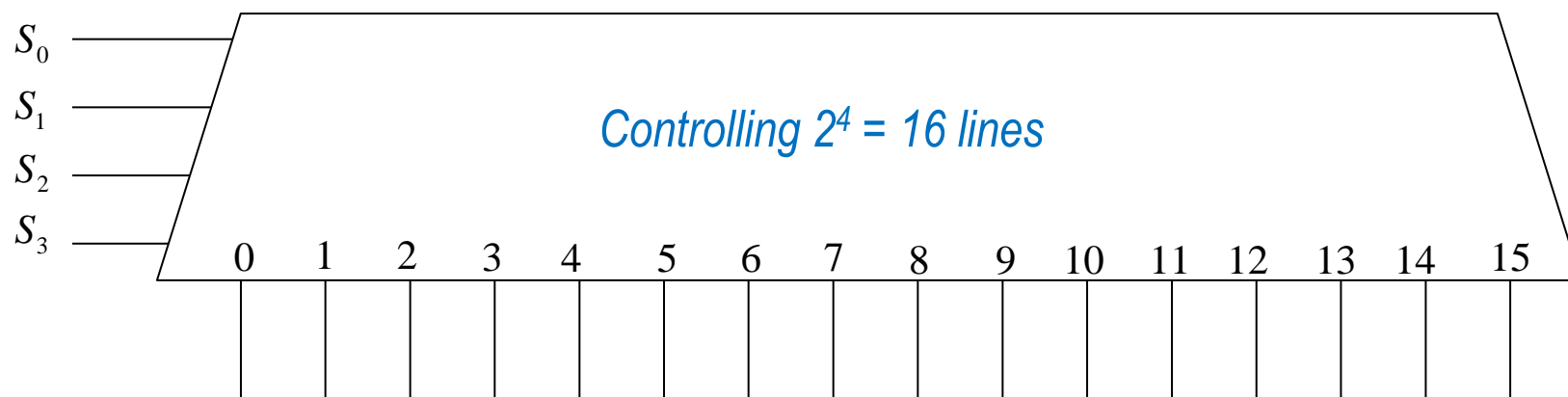


**This is how machine(computer) uses binary numbers to perform different actions!**

## ***n-bit Input Controlling/Selecting 2<sup>n</sup> Different Actions***

### ***4-bit Decode***


*4-bit binary number: 1011*

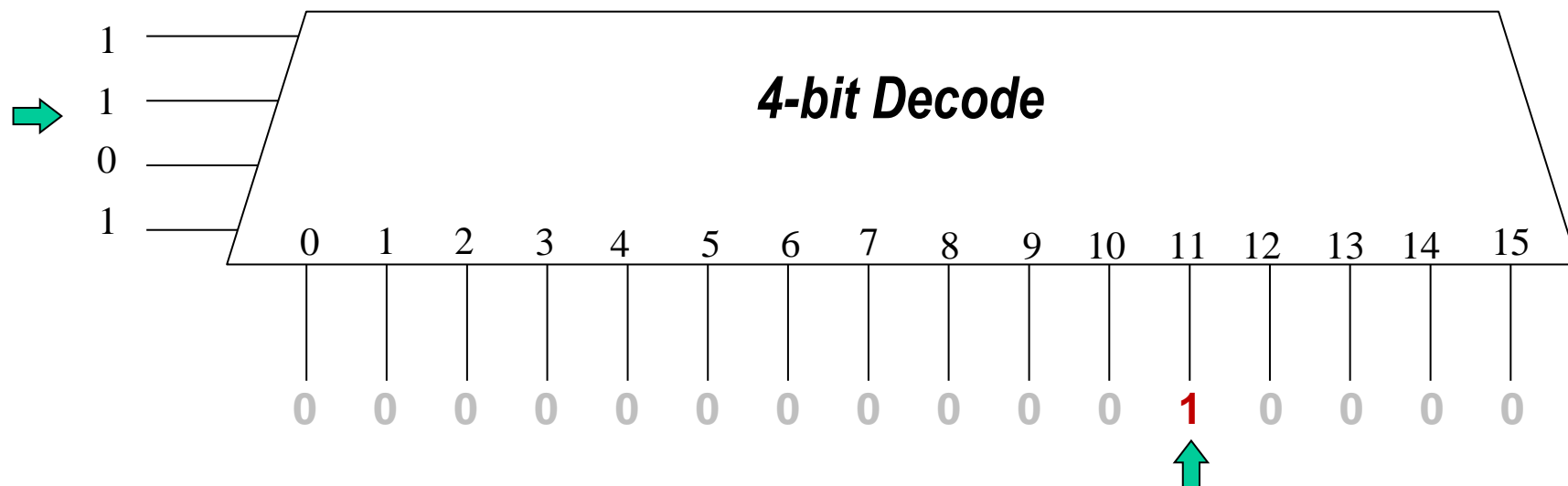

*A 4-bit binary number selects a single line (out of the 16 lines) to be “HIGH”.  
(The rest all remain “LOW”)*






## 4-bit Input Controlling/Selecting $2^4$ Different Actions

4-bit binary number 0111

 

A 4-bit binary number selects a single line (out of the 16 lines) to be "HIGH".  
(The rest all remain "LOW")

# OR Gate

     






**Truth Table**

$$C = A + B$$

Input A	Input B	Output C
0	0	0
1	0	1
0	1	1
1	1	1

$$\left\{ \begin{array}{l} 0 + 0 = 0 \\ 1 + 0 = 1 \\ 0 + 1 = 1 \\ 1 + 1 = 1 \end{array} \right.$$

# Exclusive OR Gate: XOR

     

Truth Table

$$C = A \oplus B$$

Input A	Input B	Output C
0	0	0
0	1	1
1	0	1
1	1	0


$$\left\{ \begin{array}{l} 0 \oplus 0 = 0 \\ 1 \oplus 0 = 1 \\ 0 \oplus 1 = 1 \\ 1 \oplus 1 = 0 \end{array} \right.$$

## Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r|rrrrr}
 A & & & & & \\
 + B & & & & & \\
 \hline
 & 0 & 1 & 0 & 1 & \\
 & + 0 & + 0 & + 1 & + 1 & \\
 & \hline
 & 0 & 1 & 1 & 0 &
 \end{array}$$

**Half Adder** (no input carry)

 


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 0
 \end{array}$$

**Half Adder** (no input carry)

 


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 10
 \end{array}$$

**Half Adder** (no input carry)

 

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1




# Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r}
 A \\
 + B \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 0 \\
 \hline
 0
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 0 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 0 \\
 + 1 \\
 \hline
 1
 \end{array}
 \quad
 \begin{array}{r}
 1 \\
 + 1 \\
 \hline
 1 \phantom{0} \\
 0
 \end{array}$$

**Half Adder** (no input carry)

 


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## Computing Using Logic Gates: Addition

Adding Binary Numbers for the Rightmost Digit (No Input Carry)

$$\begin{array}{r|rrrr}
 A & & & & \\
 + B & & & & \\
 \hline
 & 0 & 1 & 0 & 1 \\
 & + 0 & + 0 & + 1 & + 1 \\
 \hline
 & 0 & 1 & 1 & 0
 \end{array}$$

**Half Adder** (no input carry)

 


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Addition


Addition with input carry:

$$\begin{array}{r} 0 \\ + 0_1 \\ \hline 1 \end{array} \quad \begin{array}{r} 1 \\ + 1_0_1 \\ \hline 0 \end{array} \quad \begin{array}{r} 0 \\ + 1_1_1 \\ \hline 0 \end{array} \quad \begin{array}{r} 1 \\ + 1_1_1 \\ \hline 1 \end{array}$$


**Full Adder** (with input carry)

 

**Full Adder**

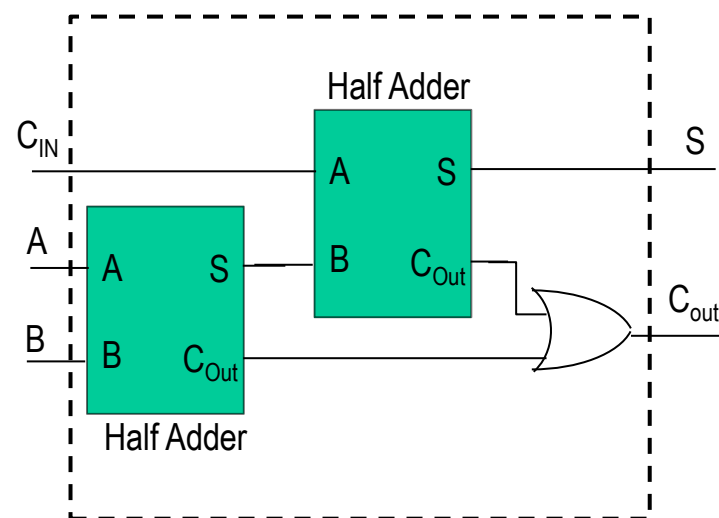


## 8-bit Adder

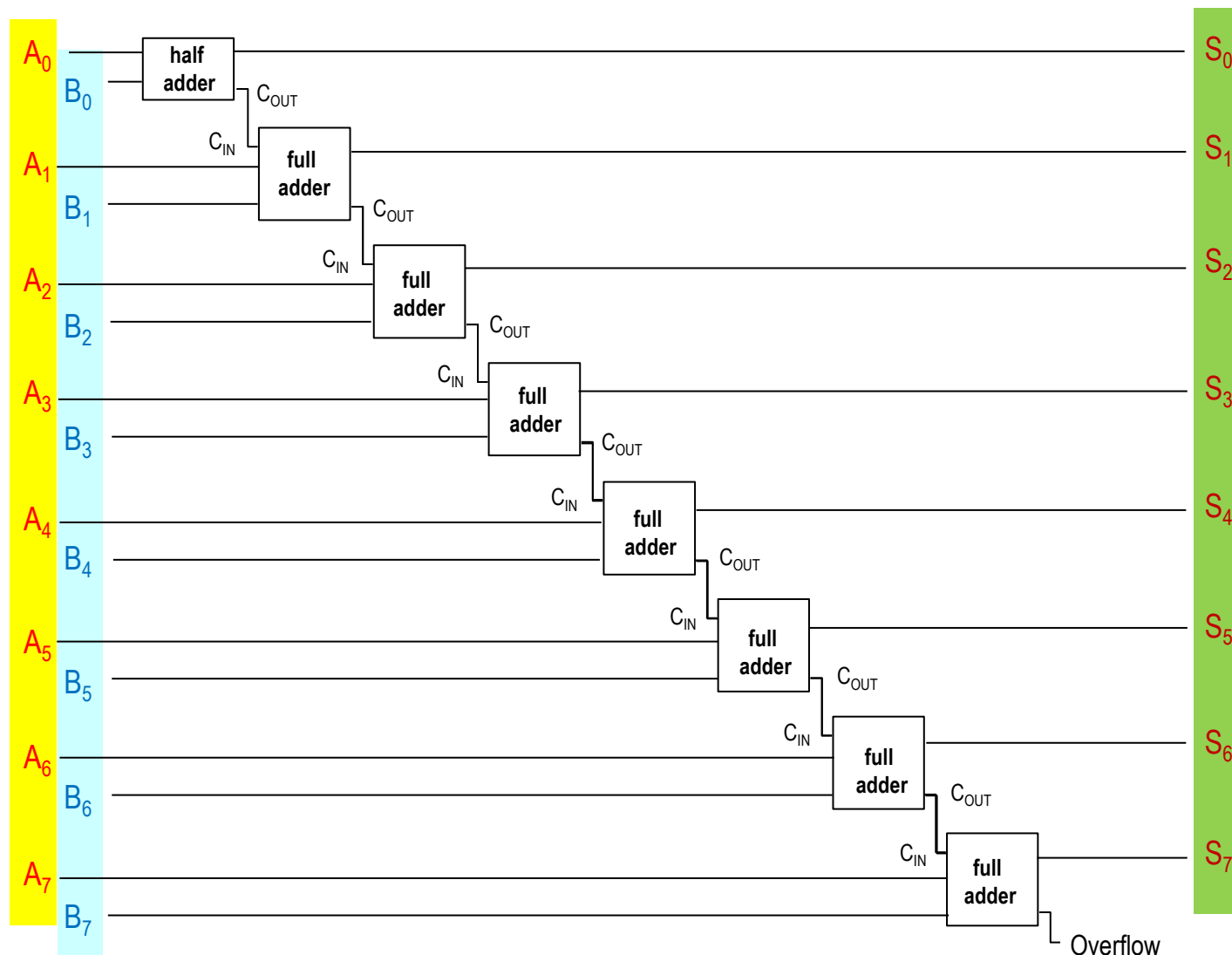


## Arithmetic Logic Unit (ALU)

---





 


# NAND Gate :

AND gate + NOT gate

 

NAND gate

     

Truth Table


$$P = \overline{A \cdot B}$$

Input A	Input B	Output P
0	0	1
1	0	1
0	1	1
1	1	0

$$\left\{ \begin{array}{l} \overline{0 \cdot 0} = \overline{0} = 1 \\ \overline{1 \cdot 0} = \overline{0} = 1 \\ \overline{0 \cdot 1} = \overline{0} = 1 \\ \overline{1 \cdot 1} = \overline{1} = 0 \end{array} \right.$$


# Boolean Algebra

## Rules

 

$X$  and  $\bar{X}$  are complements


$$\bar{\bar{X}} = X$$

 

$$0 \cdot X = 0$$

$$X \cdot \bar{X} = 0$$

$$1 \cdot X = X$$

 


$$0 + X = X$$

$$1 + X = 1$$

$$X + \bar{X} = 1$$


$$X + Y = Y + X$$

# Boolean Algebra

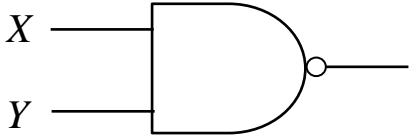


$$Z = \overline{X \cdot Y}$$
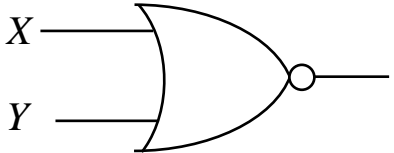
$$\left\{ \begin{array}{l} \overline{0 \cdot 0} = \overline{0} = 1 \\ \overline{1 \cdot 0} = \overline{0} = 1 \\ \overline{0 \cdot 1} = \overline{0} = 1 \\ \overline{1 \cdot 1} = \overline{1} = 0 \end{array} \right.$$



$$Z = \overline{X + Y}$$
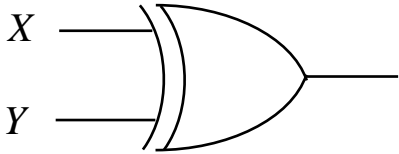
$$\left\{ \begin{array}{l} \overline{0 + 0} = \overline{0} = 1 \\ \overline{1 + 0} = \overline{1} = 0 \\ \overline{0 + 1} = \overline{1} = 0 \\ \overline{1 + 1} = \overline{1} = 0 \end{array} \right.$$



$$Z = X \oplus Y$$

$$\left\{ \begin{array}{l} 0 \oplus 0 = 0 \\ 1 \oplus 0 = 1 \\ 0 \oplus 1 = 1 \\ 1 \oplus 1 = 0 \end{array} \right.$$



## Boolean Algebra Example

## Fail-Safe Autopilot Logic

Prior to takeoff or landing maneuver, a commercial aircraft requires the following check:

**2 of the possible 3 pilots must be available: the pilot, the copilot and the autopilot**

Set Logic Variables:

$X$  – State of the pilot: 1= Present, 0=Absent

$Y$  – State of the copilot: 1= Present, 0=Absent

$Z$  – State of the autopilot: 1= Functioning, 0=Not Functioning

Logic function corresponding to “System Ready” is

$$f = X \cdot Y + X \cdot Z + Y \cdot Z$$

$f = 1$ : System Ready ;       $f = 0$ : System **Not** Ready

## Rules for Boolean Algebra

1.  $0 + X = X$

2.  $1 + X = 1$

3.  $X + X = X$

4.  $X + \bar{X} = 1$

5.  $0 \cdot X = 0$

6.  $1 \cdot X = X$

7.  $X \cdot X = X$

8.  $X \cdot \bar{X} = 0$

9.  $\bar{\bar{X}} = X$

10.  $X + Y = Y + X$

Commutative Law

11.  $X \cdot Y = Y \cdot X$

Commutative Law

12.  $X + (Y + Z) = (X + Y) + Z$



13.  $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$

14.  $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$

Distributive Law

15.  $X + X \cdot Z = X$

Absorption Law

  

## Rules for Boolean Algebra

1.  $0 + X = X$

2.  $1 + X = 1$

3.  $X + X = X$

4.  $X + \bar{X} = 1$

5.  $0 \cdot X = 0$

6.  $1 \cdot X = X$

7.  $X \cdot X = X$

8.  $X \cdot \bar{X} = 0$

9.  $\bar{\bar{X}} = X$

10.  $X + Y = Y + X$

Commutative Law

11.  $X \cdot Y = Y \cdot X$

Commutative Law

12.  $X + (Y + Z) = (X + Y) + Z$



13.  $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$

14.  $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$

Distributive Law

15.  $X + X \cdot Z = X$

Absorption Law

  

## De Morgan's Laws

---

$$\overline{(X + Y)} = \bar{X} \cdot \bar{Y}$$

$$\overline{(X \cdot Y)} = \bar{X} + \bar{Y}$$

- Any logic function can be implemented using only **OR** and **NOT** gates.
- Any logic function can be implemented using only **AND** and **NOT** gates.

## Boolean Algebra Example

## Fail-Safe Autopilot Logic

Positive check

$$f = X \cdot Y + X \cdot Z + Y \cdot Z \quad \text{sum-of-product}$$

System Not Ready Condition:

$$\overline{f} = \overline{X \cdot Y + X \cdot Z + Y \cdot Z}$$

$$= \overline{(X \cdot Y)} \cdot \overline{(X \cdot Z)} \cdot \overline{(Y \cdot Z)}$$

$$\overline{(X + Y)} = \overline{X} \cdot \overline{Y}$$

$$= (\overline{X} + \overline{Y}) \cdot (\overline{X} + \overline{Z}) \cdot (\overline{Y} + \overline{Z})$$

$$\overline{(X \cdot Y)} = \overline{X} + \overline{Y}$$

$$\overline{f} = (\overline{X} + \overline{Y}) \cdot (\overline{X} + \overline{Z}) \cdot (\overline{Y} + \overline{Z})$$